

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$a' \cdot b \cdot c \cdot d'$$

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$a' \cdot b \cdot c \cdot d'$$

$$a \cdot b' \cdot c' \cdot d'$$

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$a' \cdot b \cdot c \cdot d'$$

$$a \cdot b' \cdot c' \cdot d'$$

$$a \cdot b' \cdot c' \cdot d$$

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$a' \cdot b \cdot c \cdot d'$$

$$a \cdot b' \cdot c' \cdot d'$$

$$a \cdot b' \cdot c' \cdot d$$

$$a \cdot b' \cdot c \cdot d'$$

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$a' \cdot b \cdot c \cdot d'$$

$$a \cdot b' \cdot c' \cdot d'$$

$$a \cdot b' \cdot c' \cdot d$$

$$a \cdot b' \cdot c \cdot d'$$

$$a \cdot b' \cdot c \cdot d$$

$$a \cdot b \cdot c' \cdot d'$$

$$a \cdot b \cdot c' \cdot d$$

$$a \cdot b \cdot c \cdot d'$$

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$a' \cdot b \cdot c \cdot d'$

$a \cdot b' \cdot c' \cdot d'$

$a \cdot b' \cdot c' \cdot d$

$a \cdot b' \cdot c \cdot d'$

$a \cdot b' \cdot c \cdot d$

$a \cdot b \cdot c' \cdot d'$


$a \cdot b \cdot c' \cdot d$

$a \cdot b \cdot c \cdot d'$

or

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

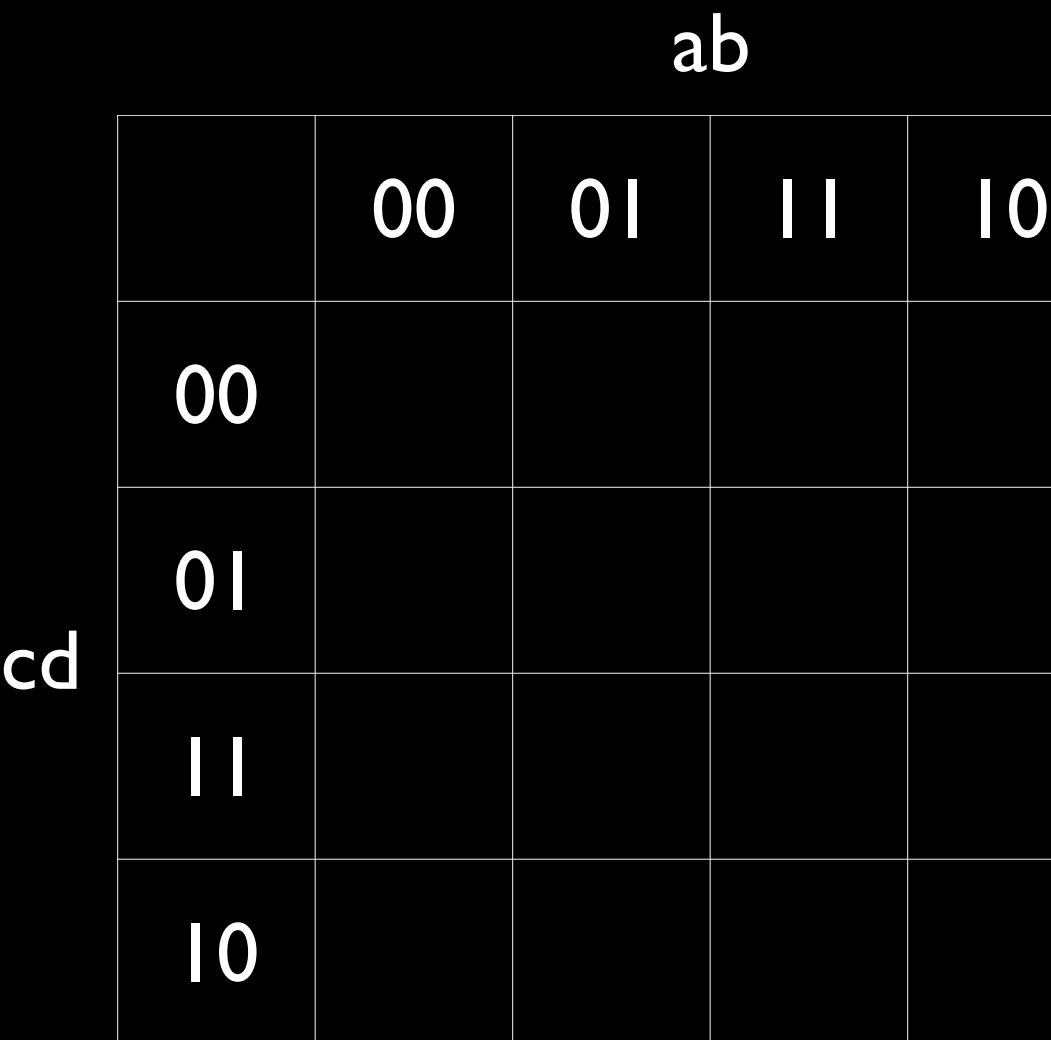

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0




Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0




Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

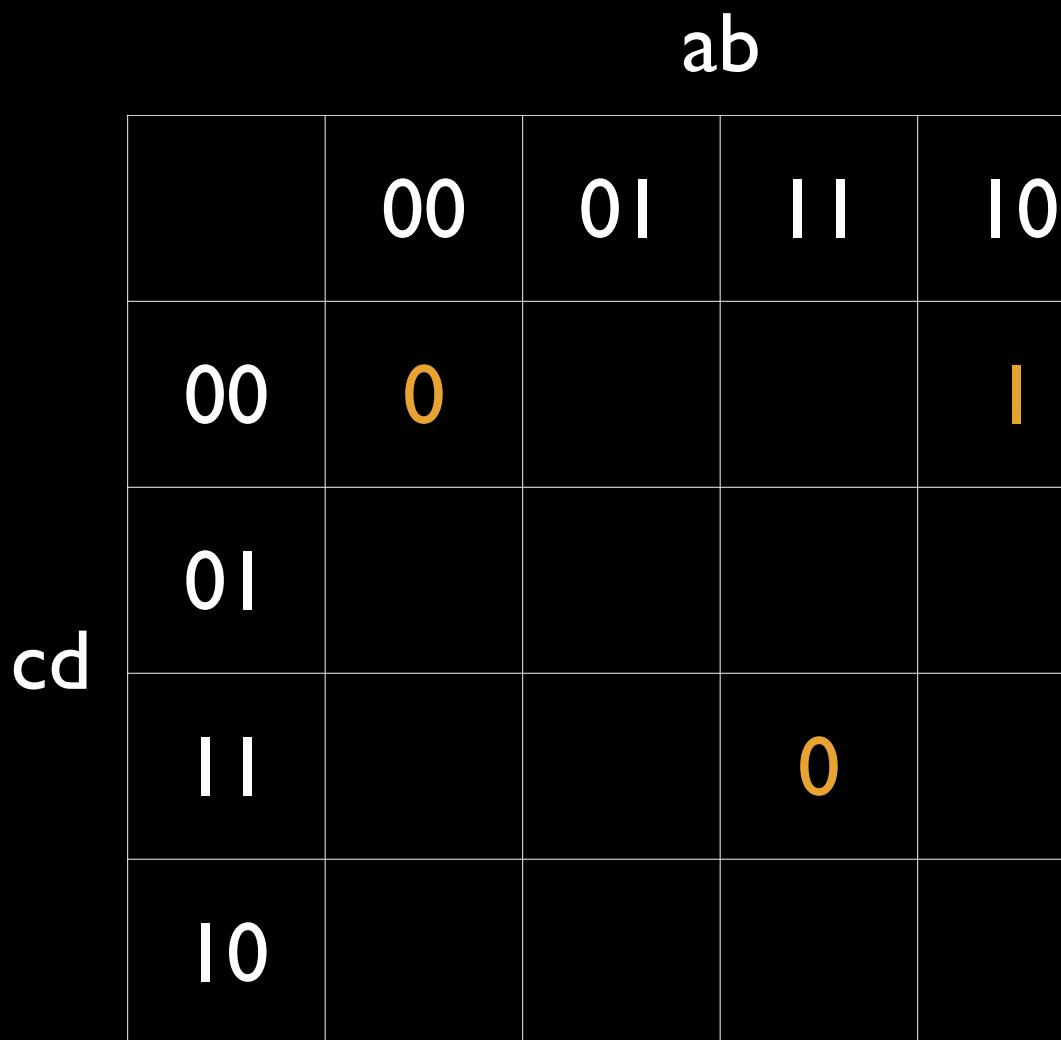

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

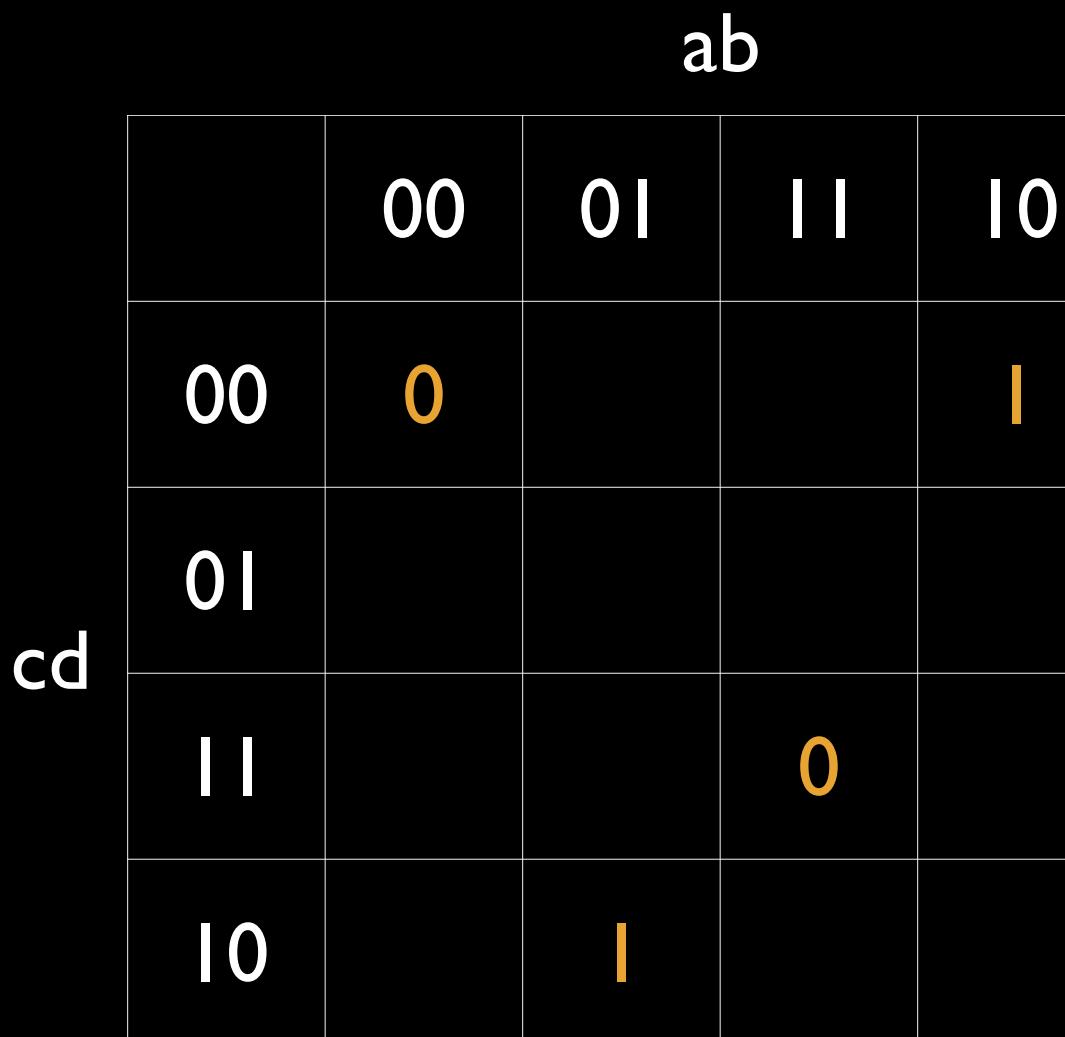

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0


ab

	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	0	1
10	0	1	1	1

cd


Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

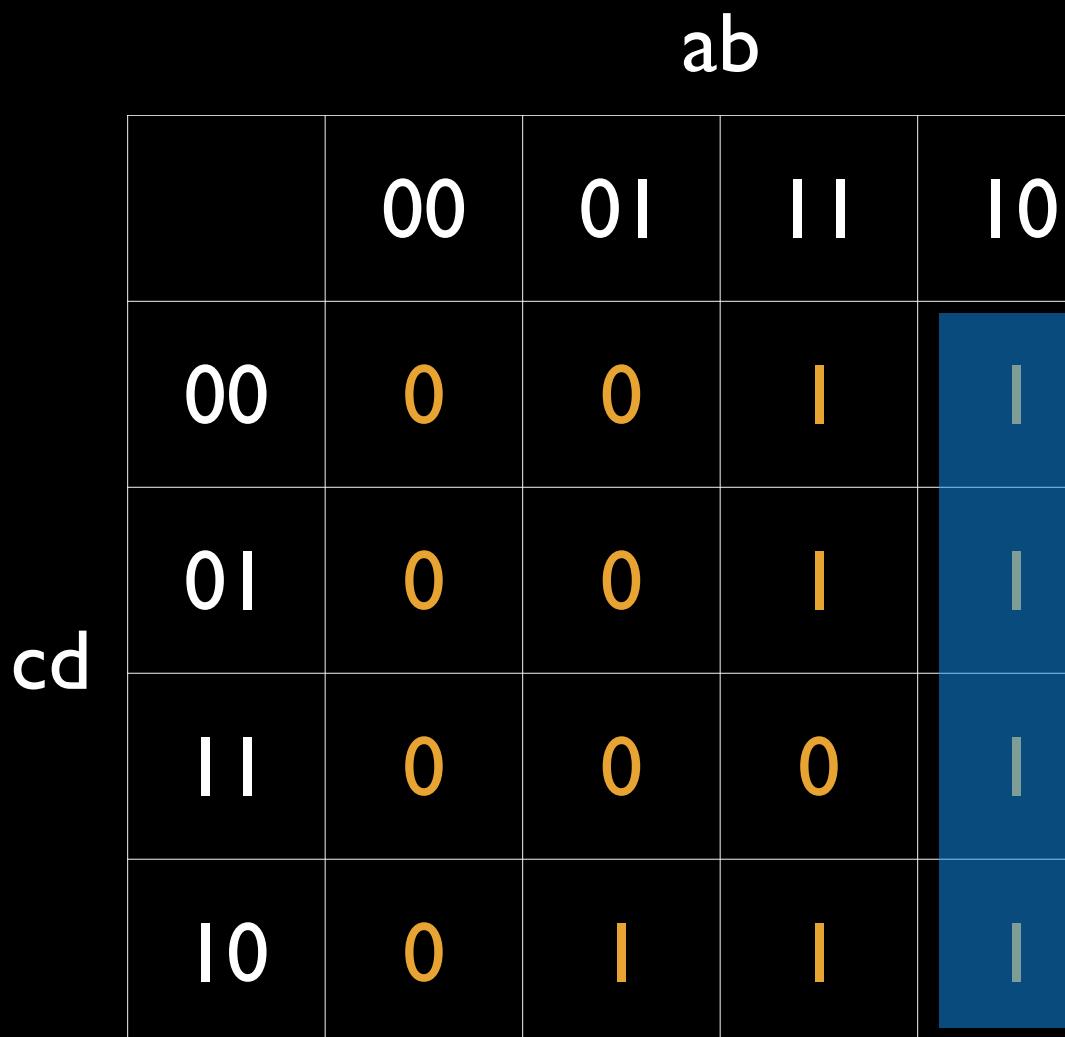


Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

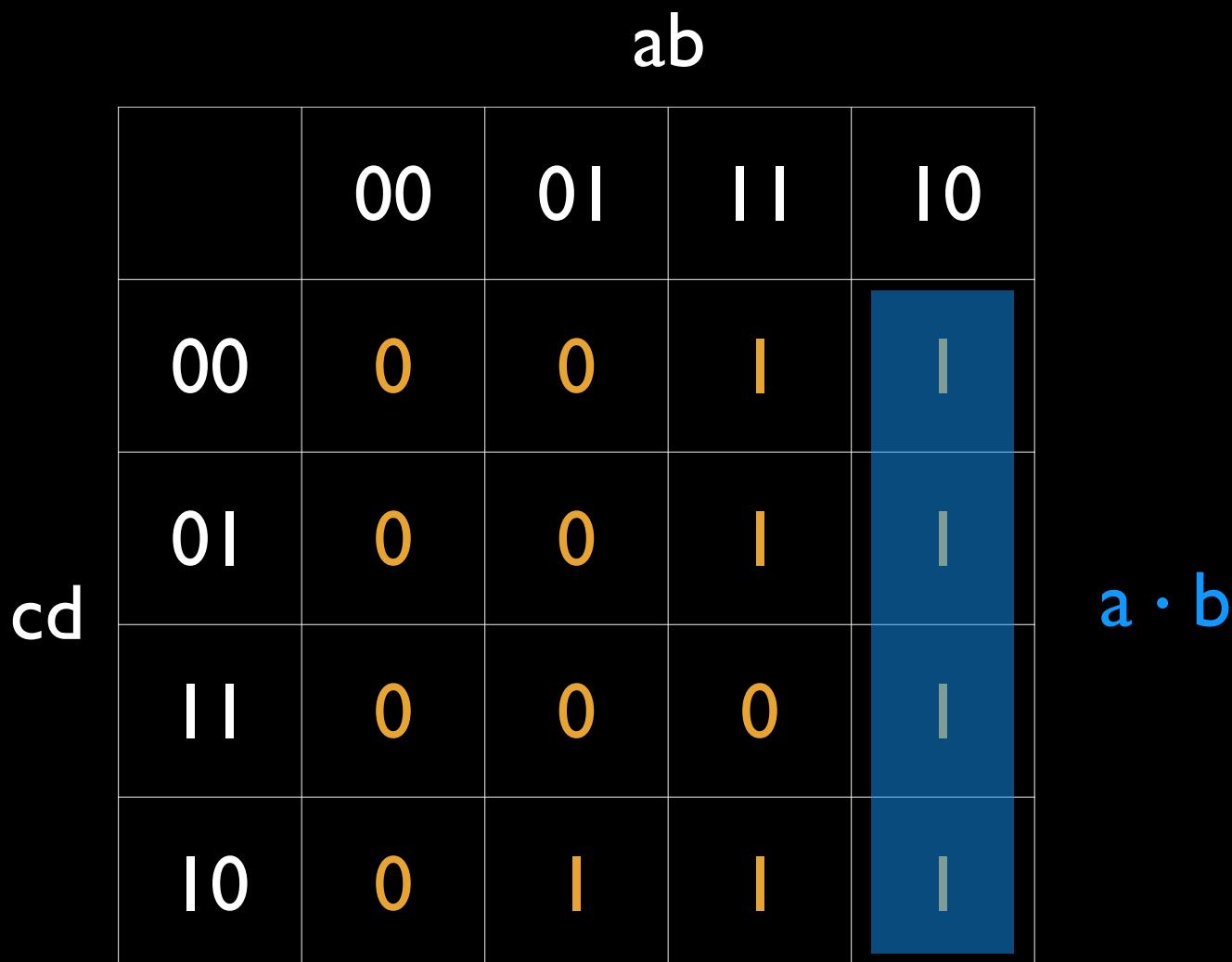

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

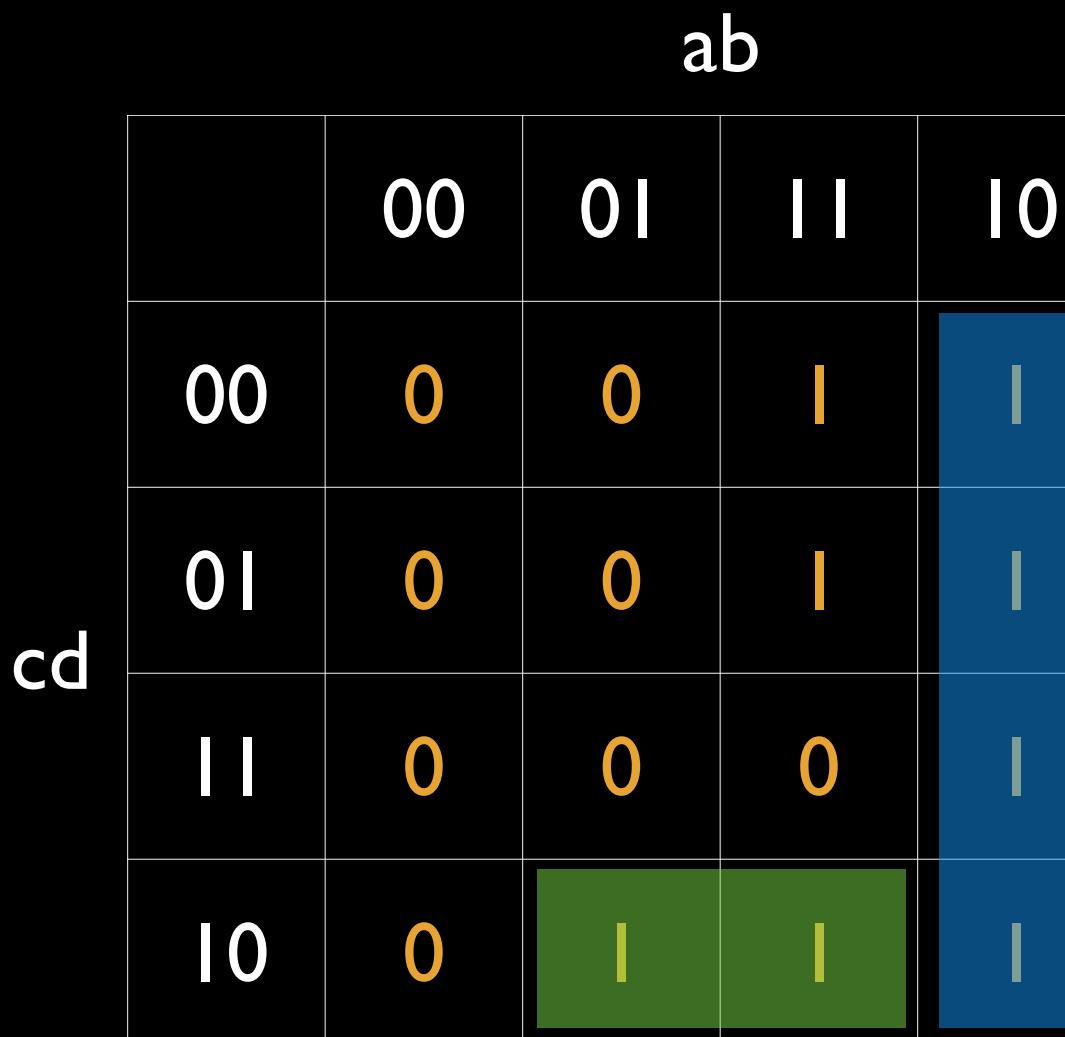


Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0




Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

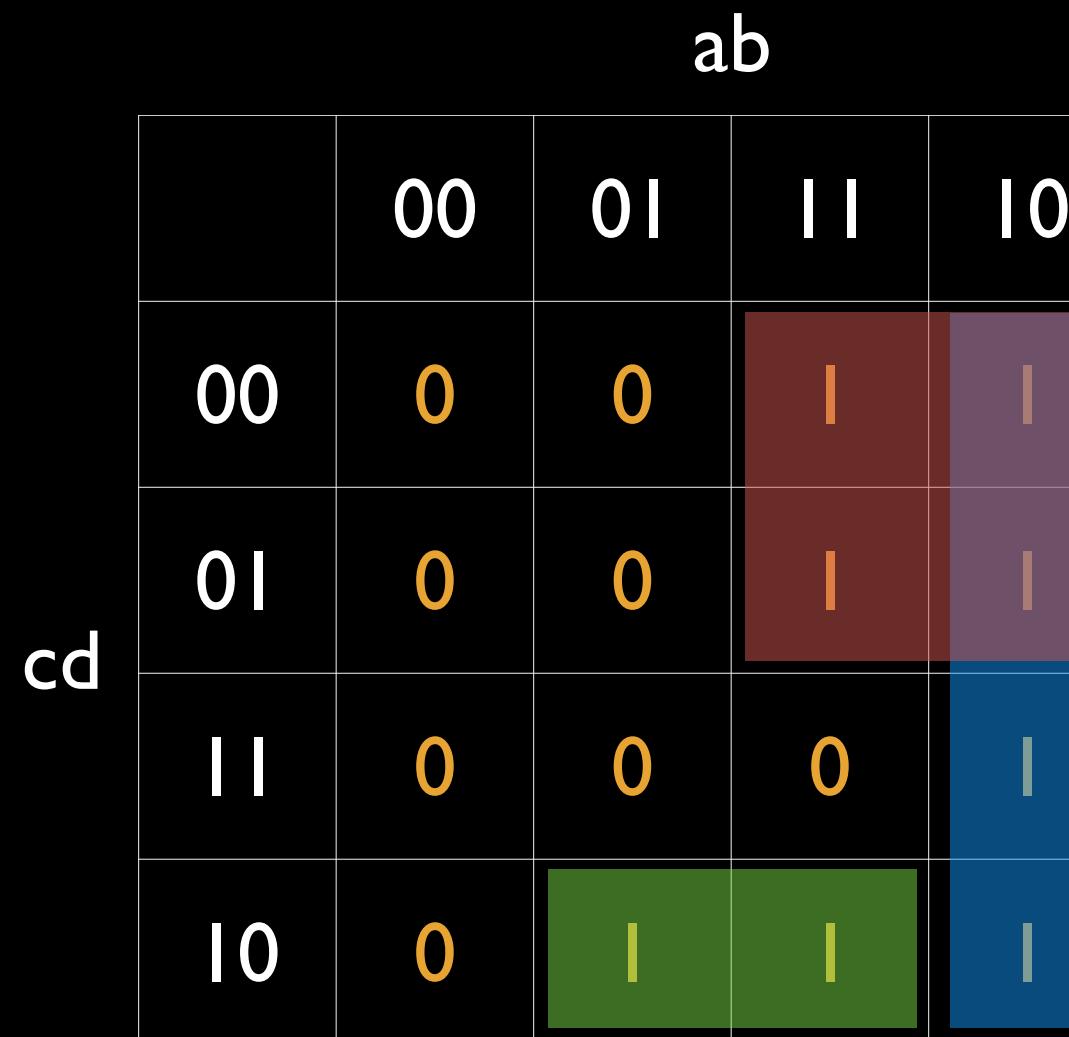


Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

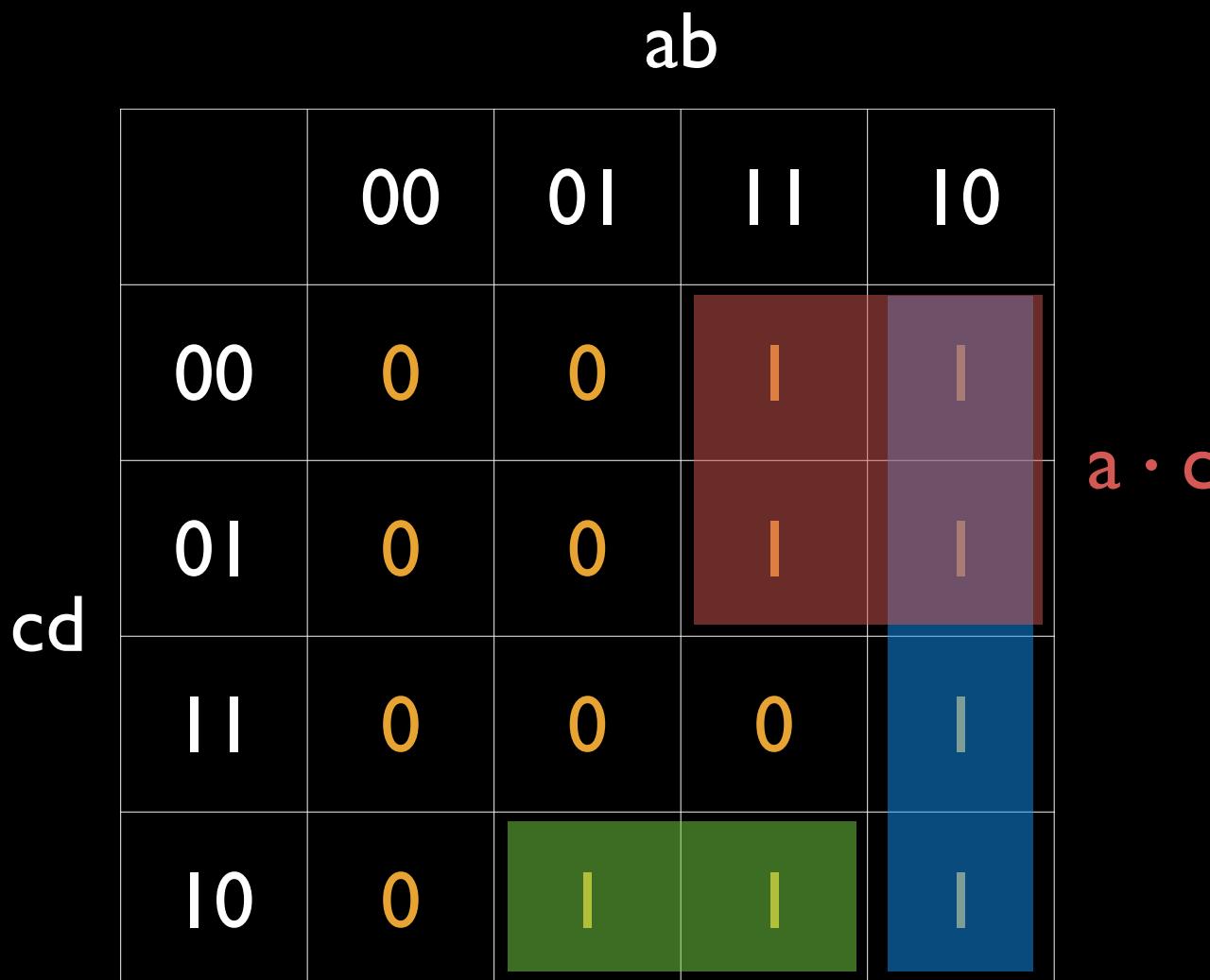

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

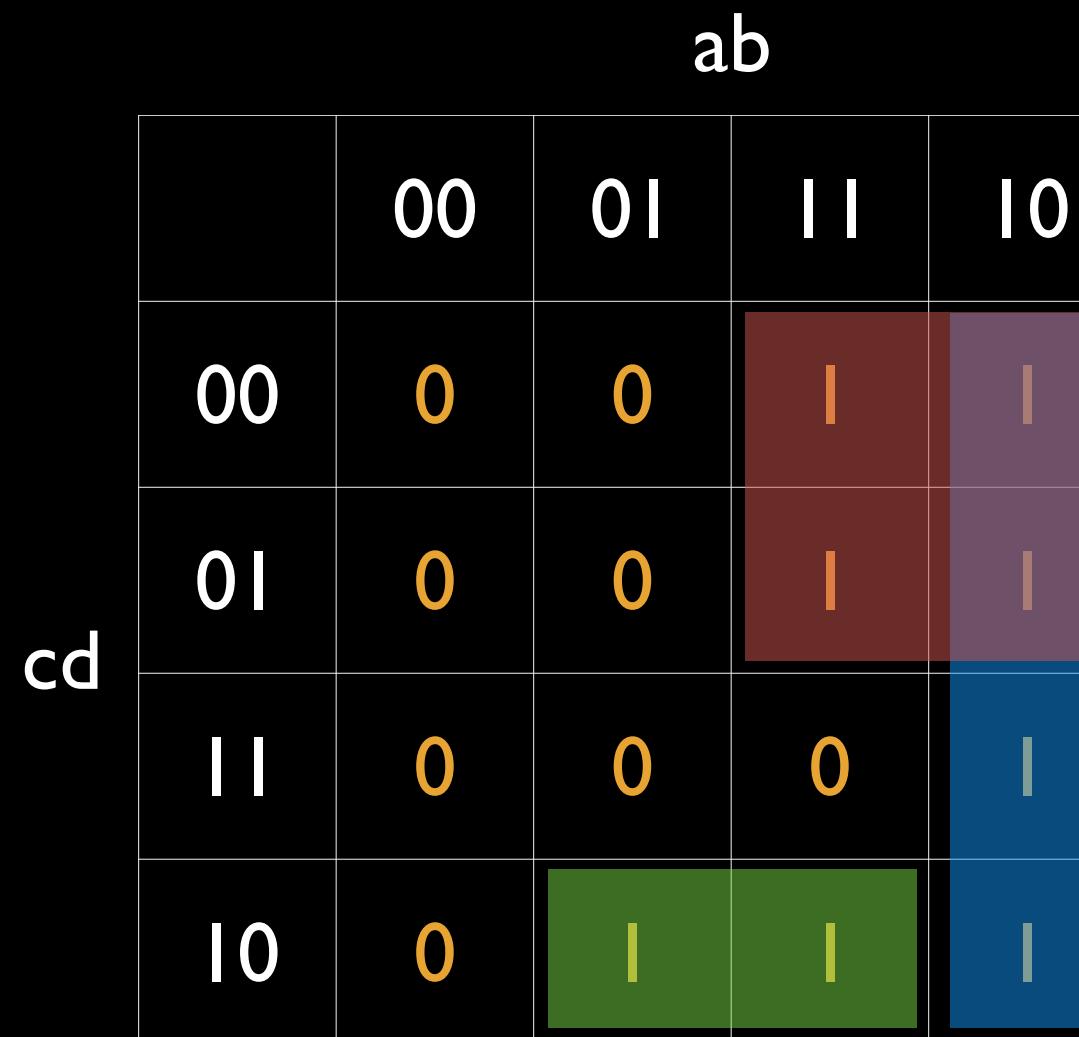

$$e = a \cdot b' + b \cdot c \cdot d' + a \cdot c'$$

Optimization (Karnaugh maps)

a	b	c	d	e
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$a' \cdot b \cdot c \cdot d'$$

$$a \cdot b' \cdot c' \cdot d'$$

$$a \cdot b' \cdot c' \cdot d$$

$$a \cdot b' \cdot c \cdot d'$$

$$a \cdot b' \cdot c \cdot d$$

$$a \cdot b \cdot c' \cdot d'$$


$$a \cdot b \cdot c' \cdot d$$

$$a \cdot b \cdot c \cdot d'$$


Circuits

A **circuit** is a collection of logical gates that transforms a set of binary inputs into a set of binary outputs.

Circuits

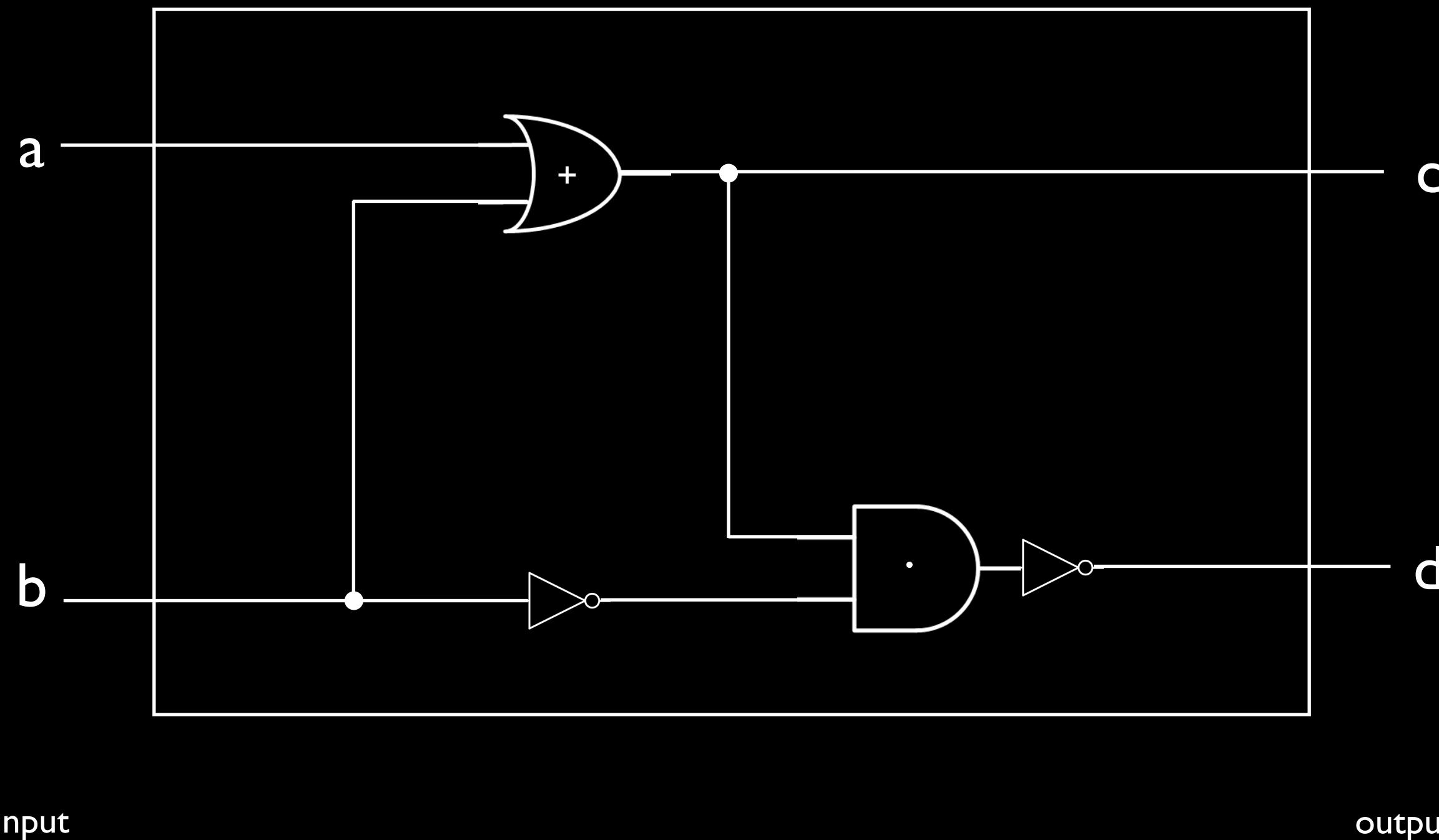


Circuits

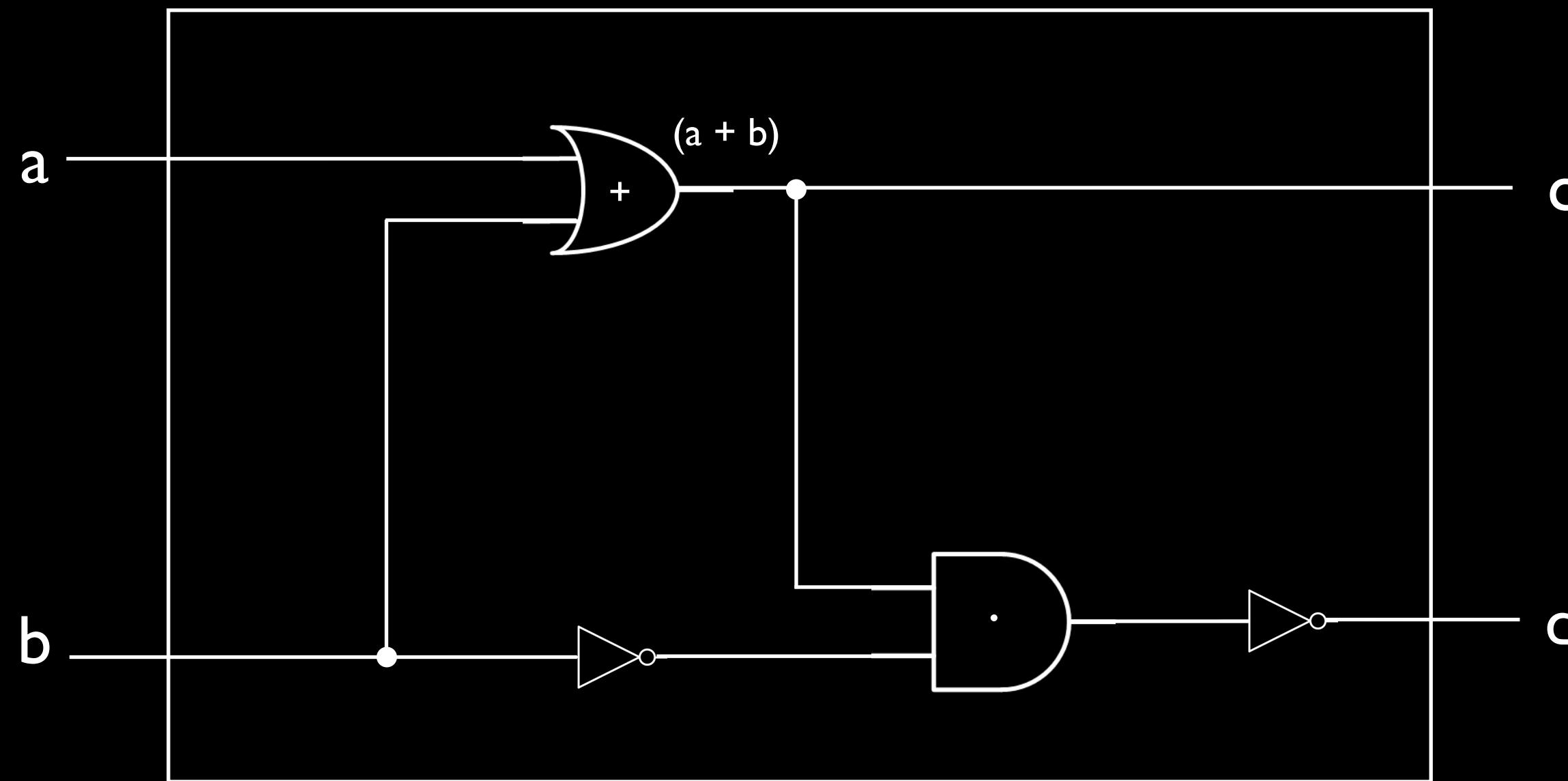


$$c = (a + b)$$

Circuits

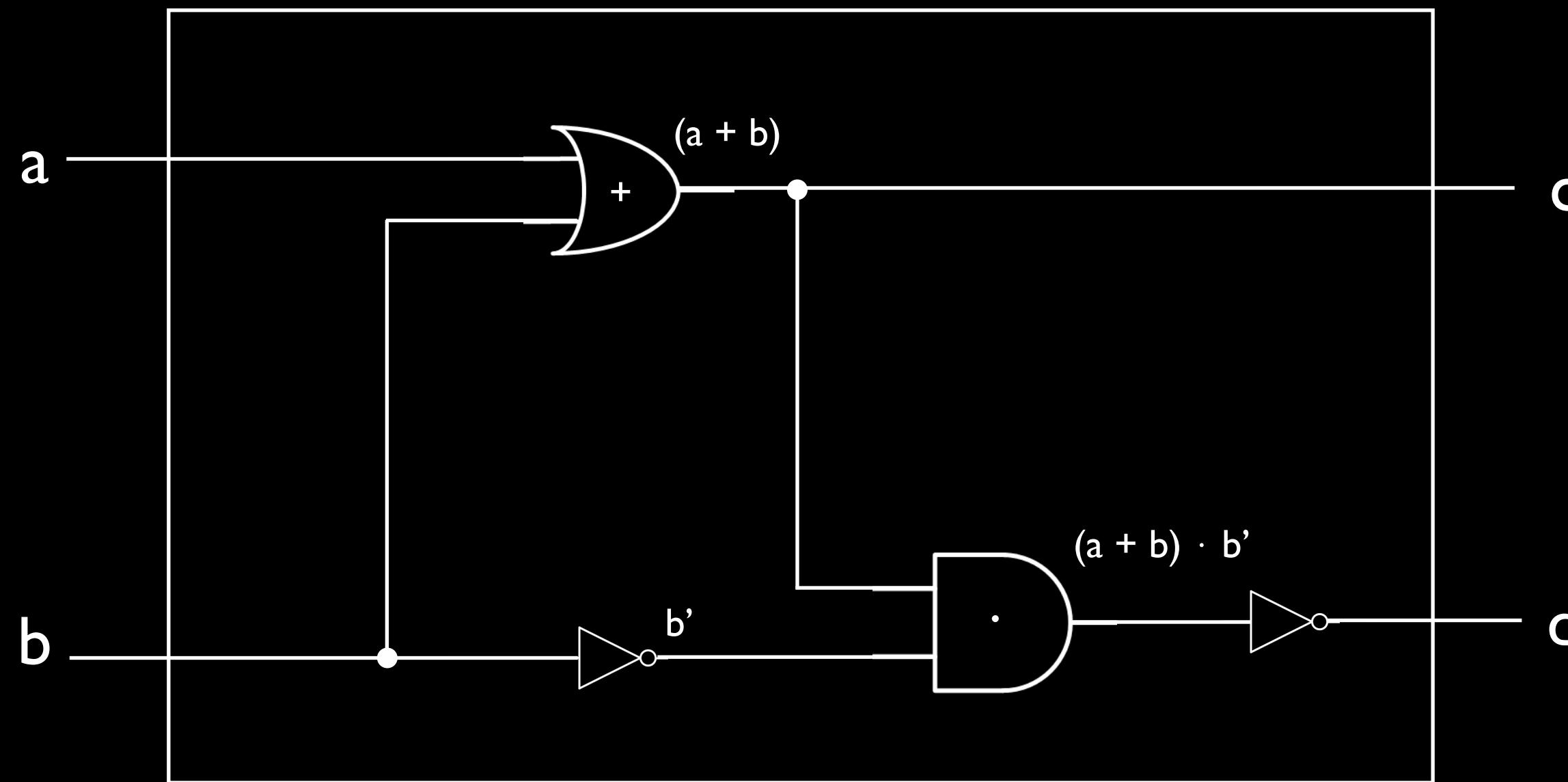

Circuits

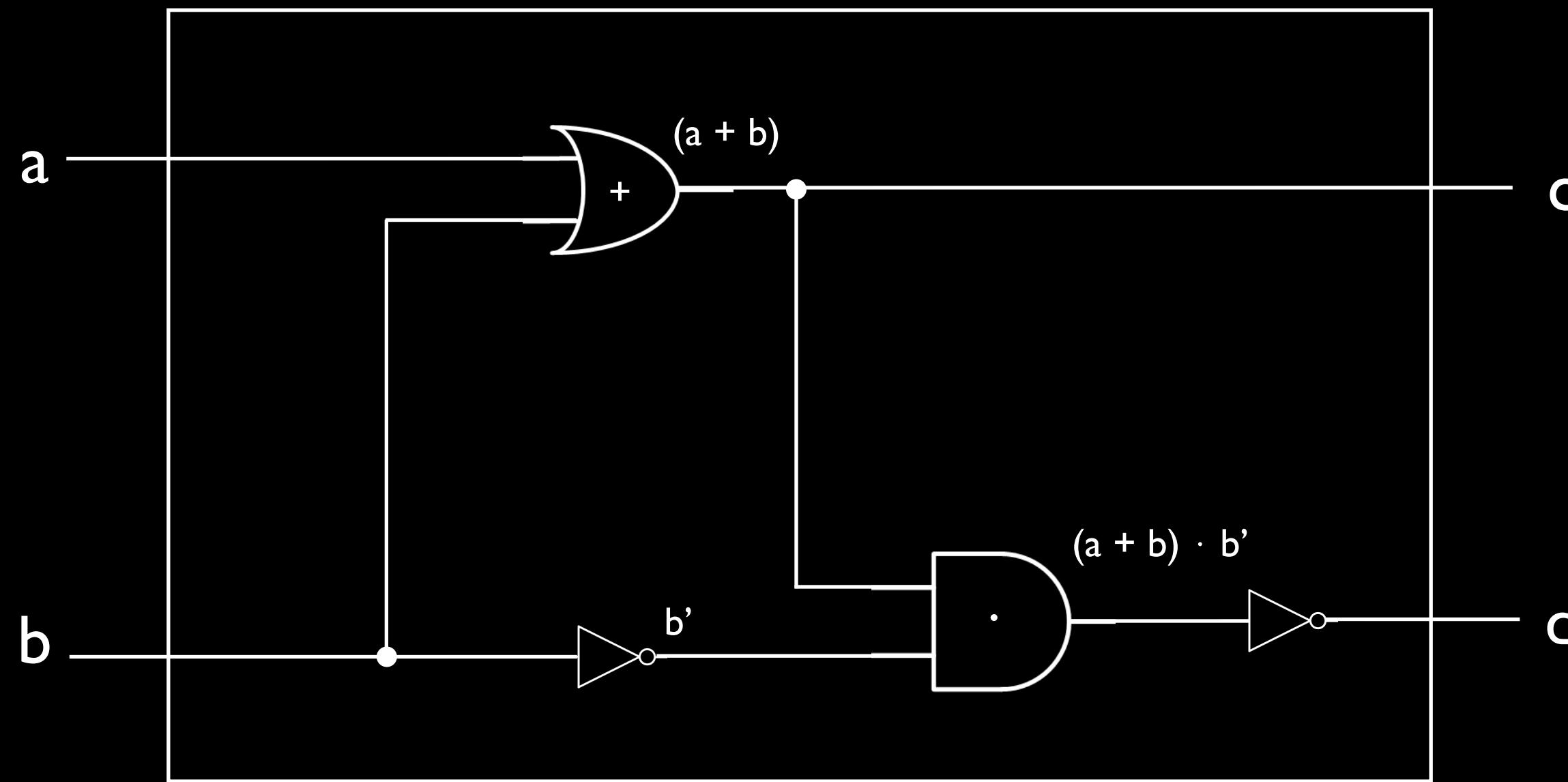

$$d = ((a + b) \cdot b')'$$

Designing Circuits

input		output	
a	b	c	d
0	0		
0			
	0		

step I. build truth-table for all possible input/output values

Designing Circuits

input				output
a	b	c	d	
0	0	0	0	
0			0	
	0		0	
		0		

arbitrary, for now

step I. build truth-table for all possible input/output values

Designing Circuits

input		output	
a	b	c	d
0	0	0	0
0			0
	0		0
		0	

arbitrary, for now

step 2. build sub-expressions with *and/not* for each output column

Designing Circuits

input		output	
a	b	c	d
0	0	0	0
0	I	I	0
I	0	I	0
I	I	0	I

$$d = a \cdot b$$

step 2. build sub-expressions with *and/not* for each output column

Designing Circuits

input	output		
a	b	c	d
0	0	0	0
0			0
	0		0
		0	

$$c = a' \cdot b$$

step 2. build sub-expressions with *and/not* for each output column

Designing Circuits

input		output	
a	b	c	d
0	0	0	0
0			0
	0		0
		0	

$$c = a' \cdot b$$

$$c = a \cdot b'$$

step 2. build sub-expressions with *and/not* for each output column

Designing Circuits

input		output	
a	b	c	d
0	0	0	0
0	I	I	0
I	0	I	0
I	I	0	I

step 3. combine, two at a time, sub-expressions with an *or*

Designing Circuits

input		output	
a	b	c	d
0	0	0	0
0	I	I	0
I	0	I	0
I	I	0	I

$$c = (a' \cdot b) + (a \cdot b')$$

step 3. combine, two at a time, sub-expressions with an *or*

Designing Circuits


input	output		
a	b	c	d
0	0	0	0
0	I	I	0
I	0	I	0
I	I	0	I

$$c = (a' \cdot b) + (a \cdot b')$$

$$d = a \cdot b$$

step 3. combine, two at a time, sub-expressions with an *or*

Designing Circuits

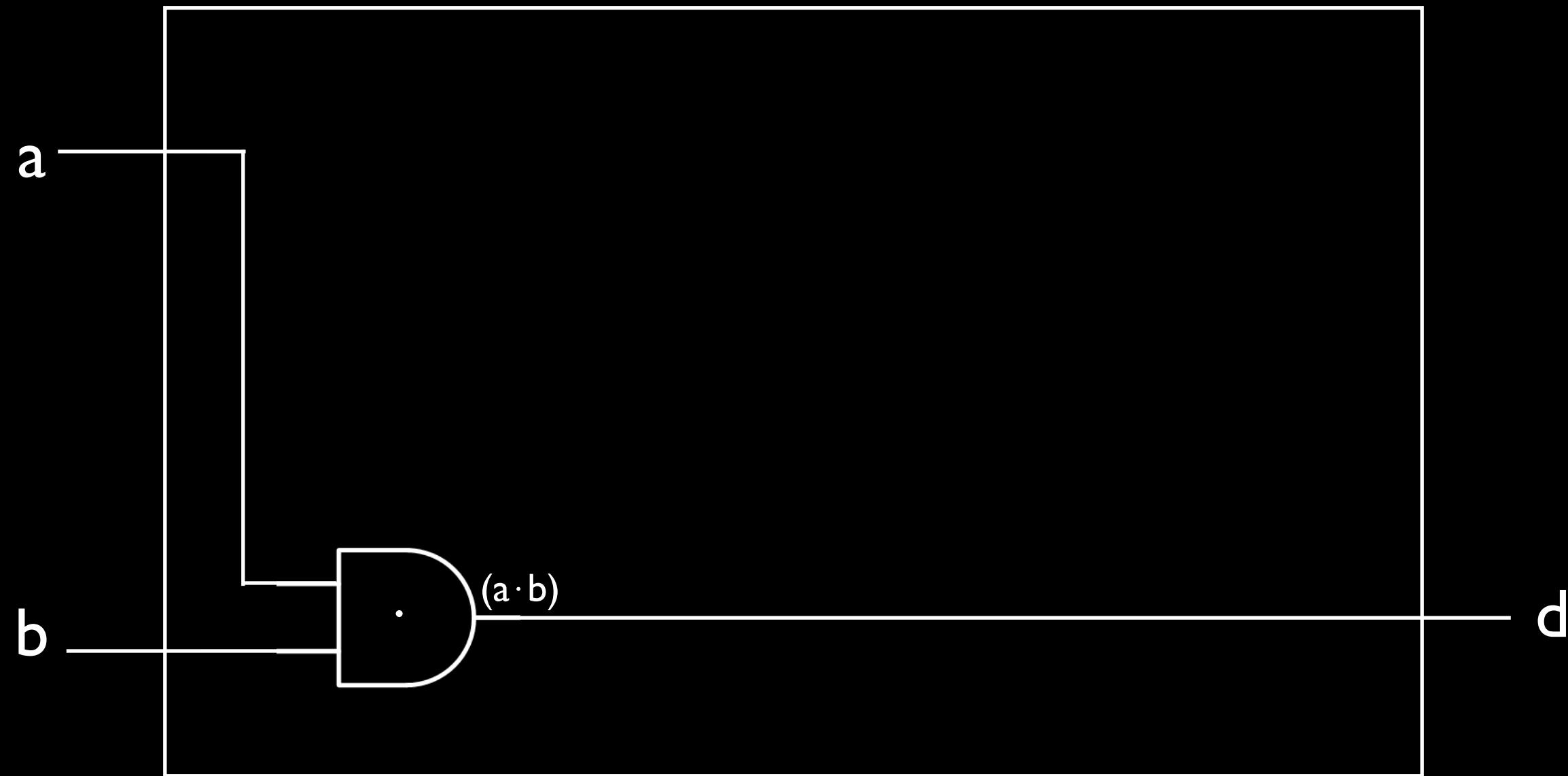


$$d = a \cdot b$$

step 4. draw circuit diagram

Designing Circuits


$$c = (a' \cdot b) + (a \cdot b')$$

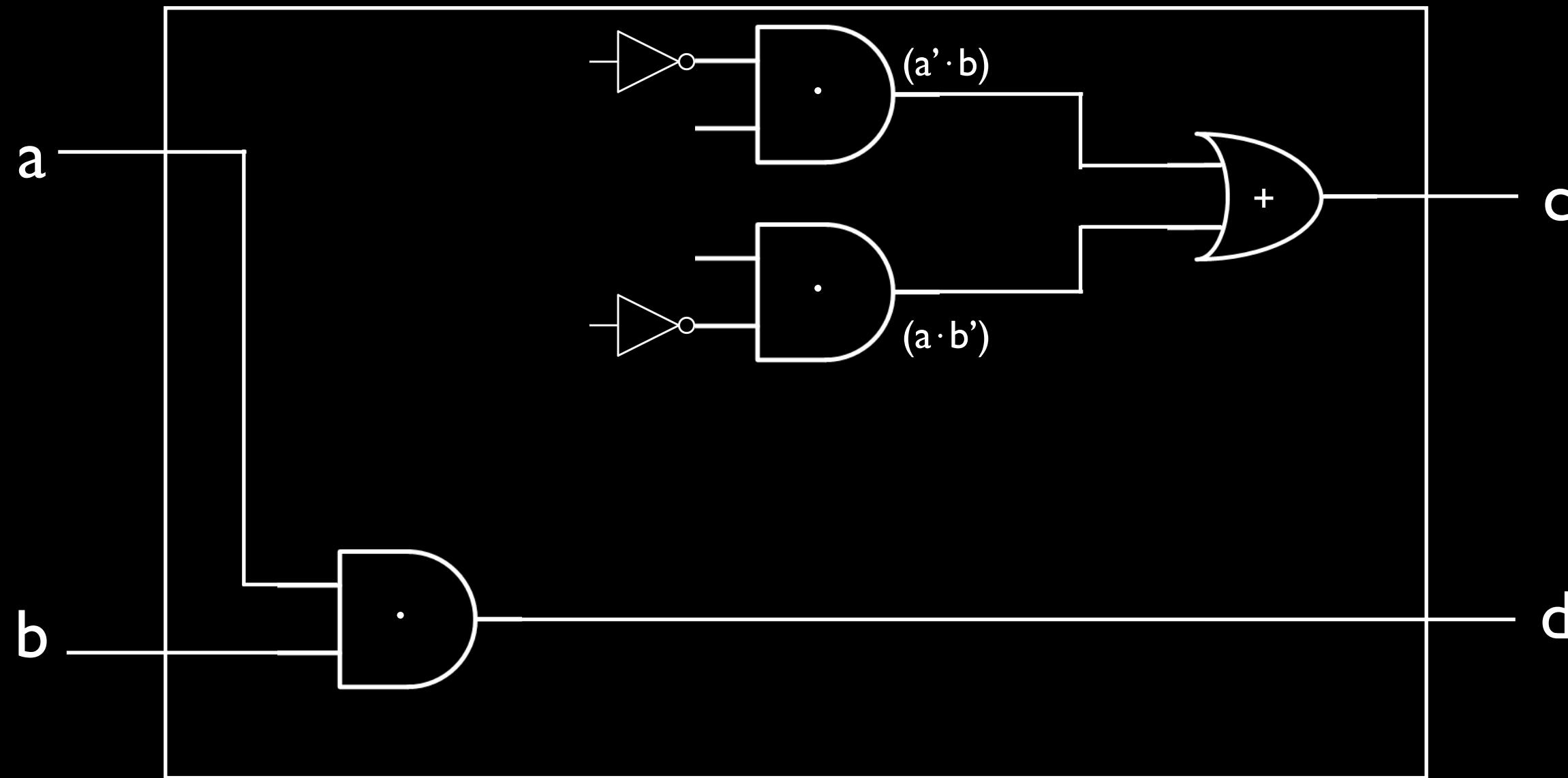

step 4. draw circuit diagram

Designing Circuits

$$c = (a' \cdot b) + (a \cdot b')$$

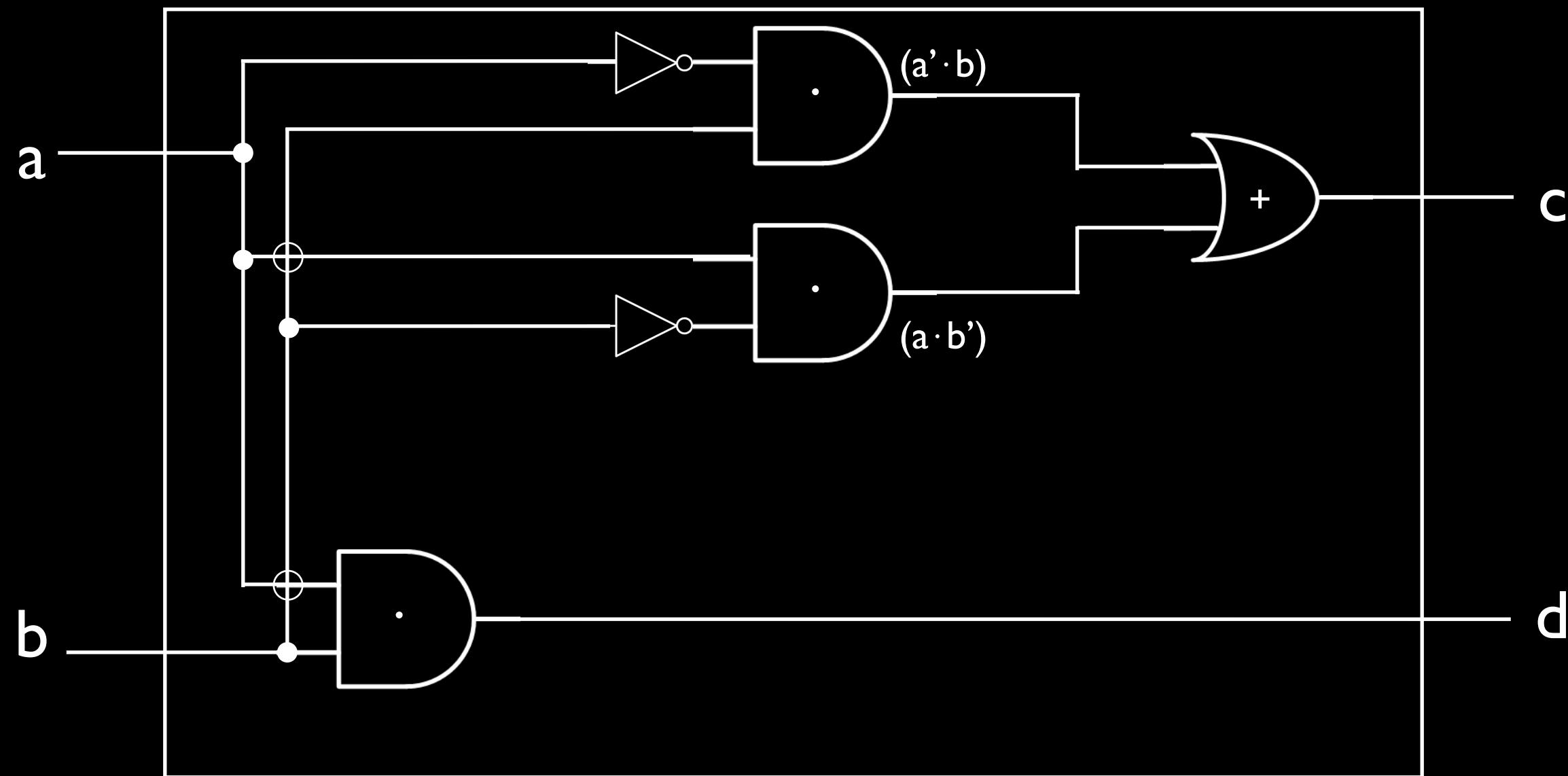

step 4. draw circuit diagram

Designing Circuits

step 1. build truth-table for all possible input/output values

step 2. build sub-expressions with *and/not* for each output column

step 3. combine, two at a time, sub-expressions with an *or*

step 4. draw circuit diagram

I-Bit Compare for Equality (CE)

```
If two bits a, b are equal then  
    return 1  
else  
    return 0
```

I-Bit Compare for Equality (CE)

input	output	
a	b	c
0	0	
0	1	
1	0	
1	1	

I-Bit Compare for Equality (CE)

input	output	
a	b	c
0	0	I
0	I	0
I	0	0
I	I	I

I-Bit Compare for Equality (CE)

input	output		
a	b	c	sub-expression
0	0	I	
0	I	0	
I	0	0	
I	I	I	

I-Bit Compare for Equality (CE)


input	input	input	output
a	b	c	sub-expression
0	0		$a' \cdot b'$
0		0	
	0	0	
			$a \cdot b$

I-Bit Compare for Equality (CE)

input			output
a	b	c	sub-expression
0	0	I	$a' \cdot b'$
0	I	0	
I	0	0	
I	I	I	$a \cdot b$


$$c = (a' \cdot b') + (a \cdot b)$$

1-Bit Compare for Equality (CE)

 


$$c = (a' \cdot b') + (a \cdot b)$$

1-Bit Compare for Equality (CE)

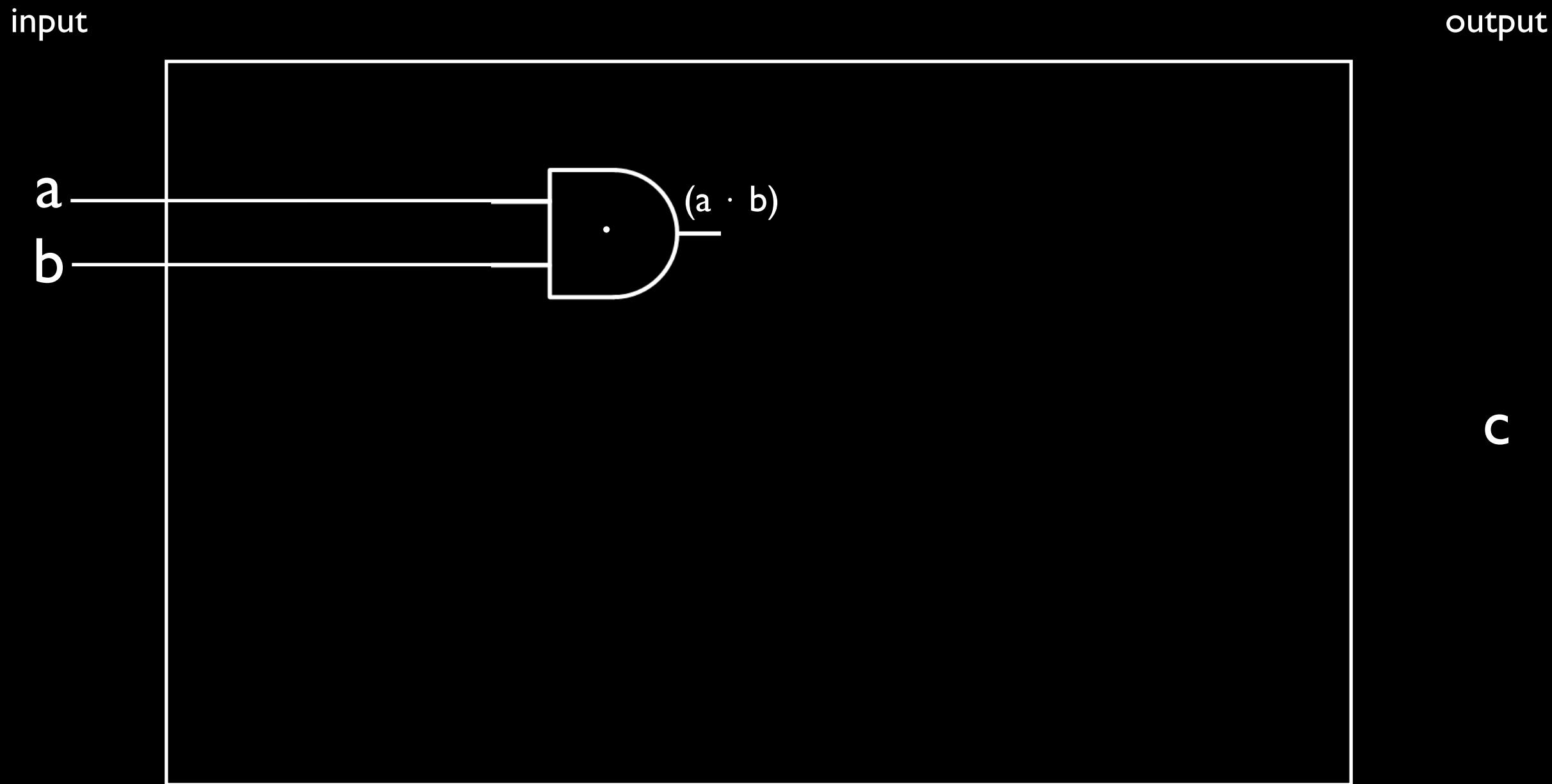


$$c = (a' \cdot b') + (a \cdot b)$$

1-Bit Compare for Equality (CE)

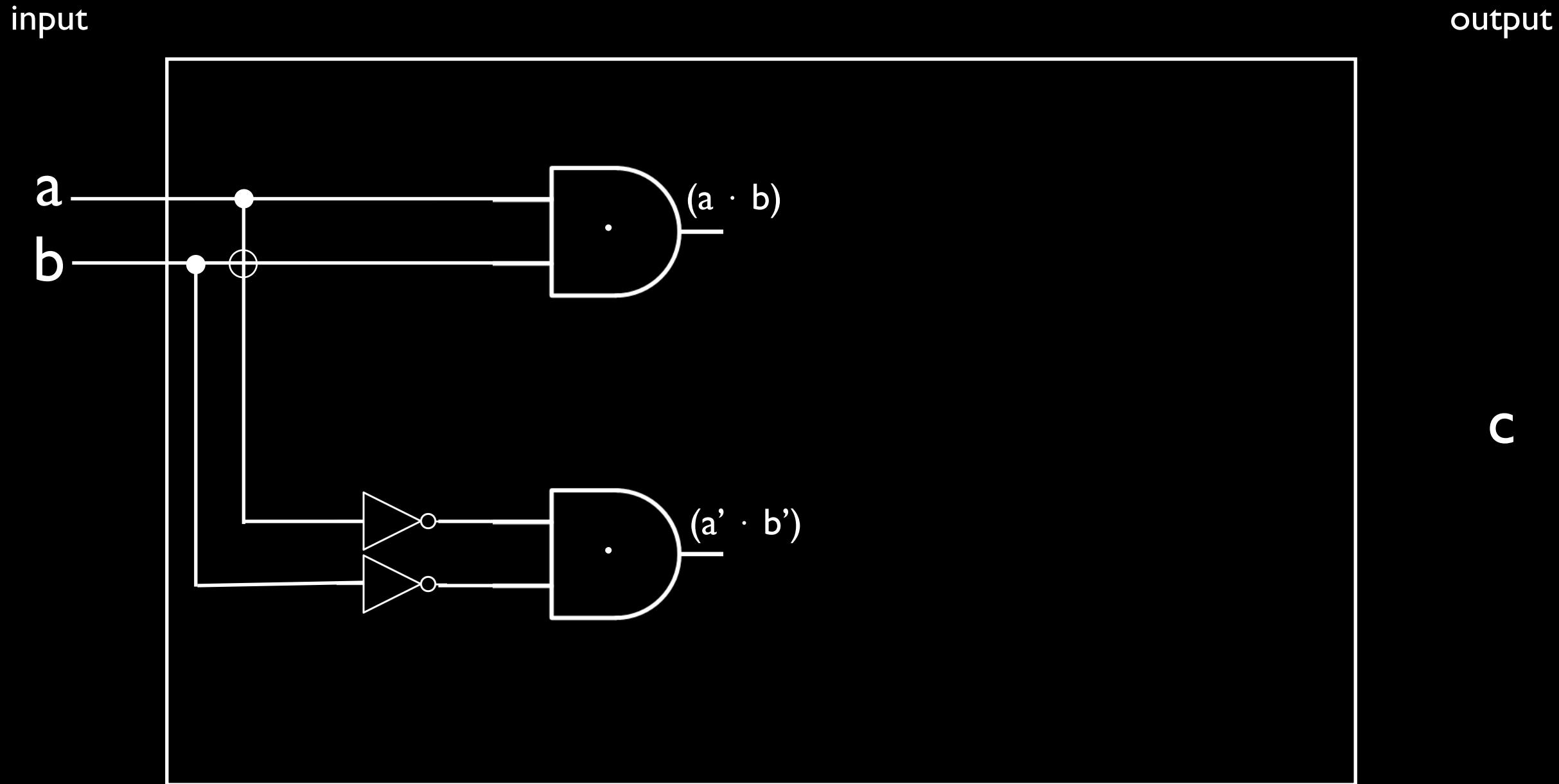

$$c = (a' \cdot b') + (a \cdot b)$$

1-Bit Compare for Equality (CE)

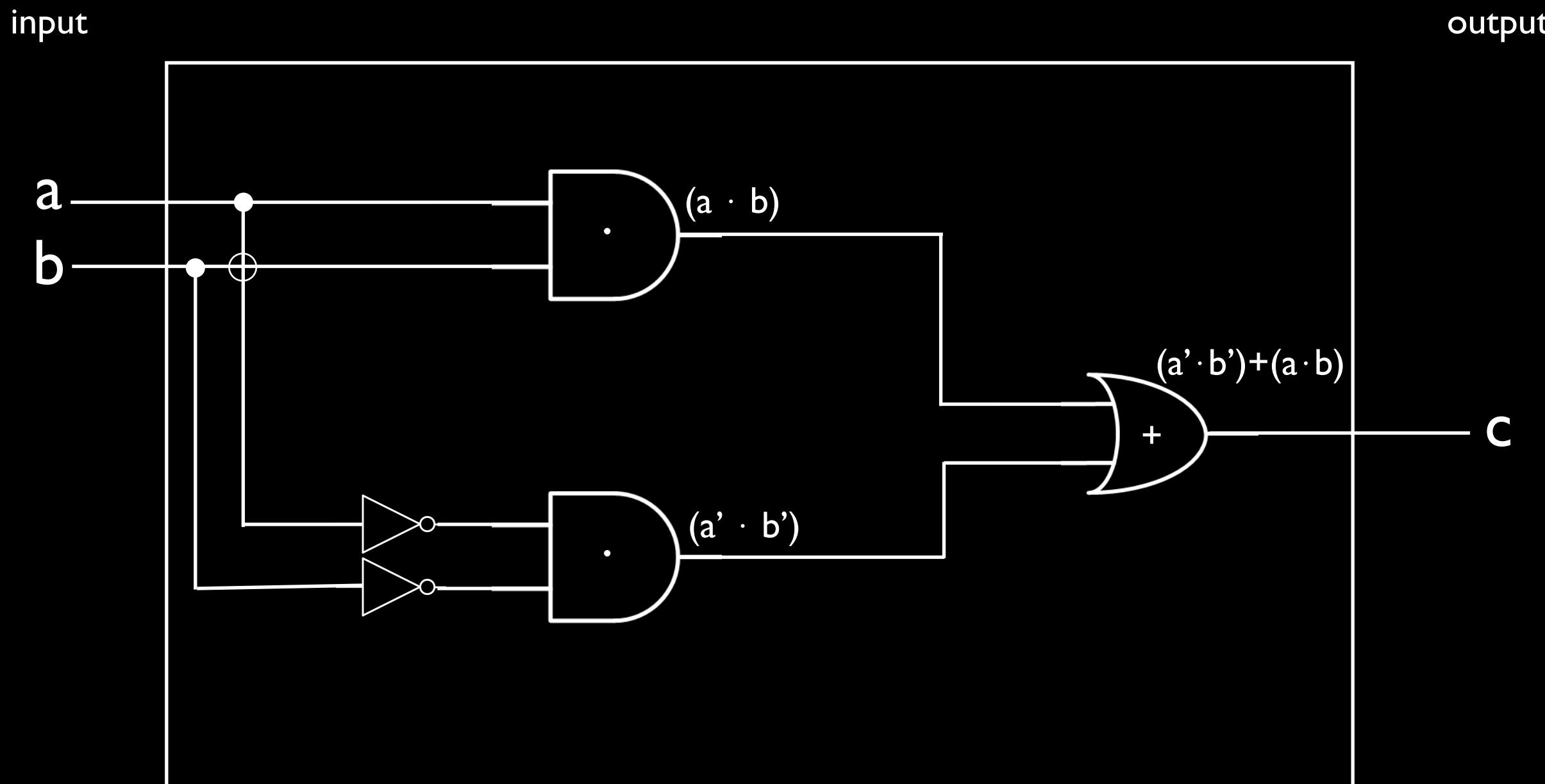

$$c = (a' \cdot b') + (a \cdot b)$$

4-Bit Compare for Equality (CE)

```
If two 4-bit numbers are equal then  
    return 1  
else  
    return 0
```

4-Bit Compare for Equality (CE)

```
If two 4-bit numbers are equal then  
    return 1  
else  
    return 0
```

$$a_3 \ a_2 \ a_1 \ a_0 == b_3 \ b_2 \ b_1 \ b_0$$

4-Bit Compare for Equality (CE)

input								output
a ₃	a ₂	a ₁	a ₀	b ₃	b ₂	b ₁	b ₀	c

how many rows?

4-Bit Compare for Equality (CE)



4-Bit Compare for Equality (CE)

two 4-bit numbers are equal if:

$a_3 == b_3$ and


$a_2 == b_2$ and

$a_1 == b_1$ and


$a_0 == b_0$

$a_3 \ a_2 \ a_1 \ a_0 == b_3 \ b_2 \ b_1 \ b_0$

4-Bit Compare for Equality (CE)

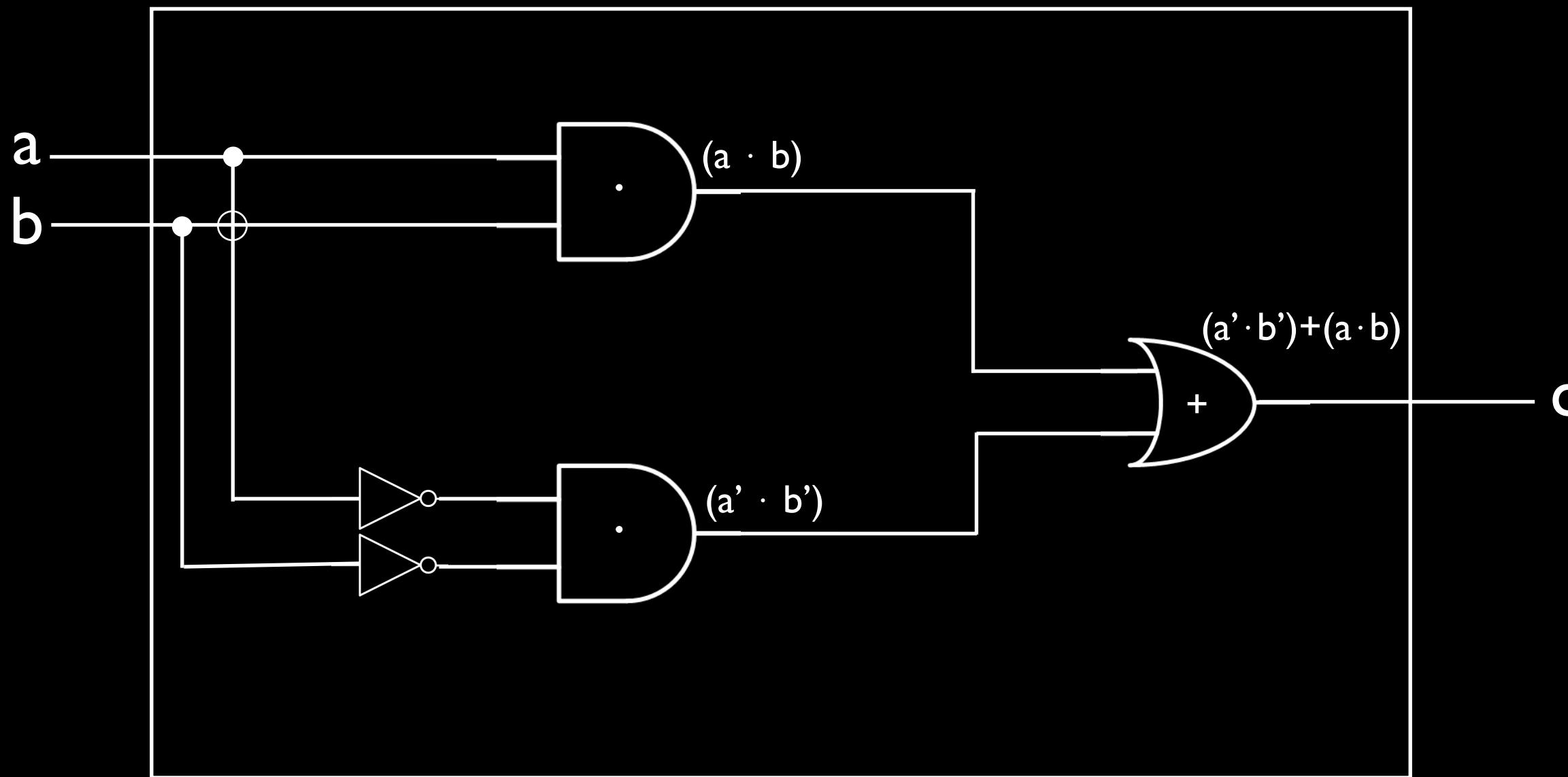


4-Bit Compare for Equality (CE)

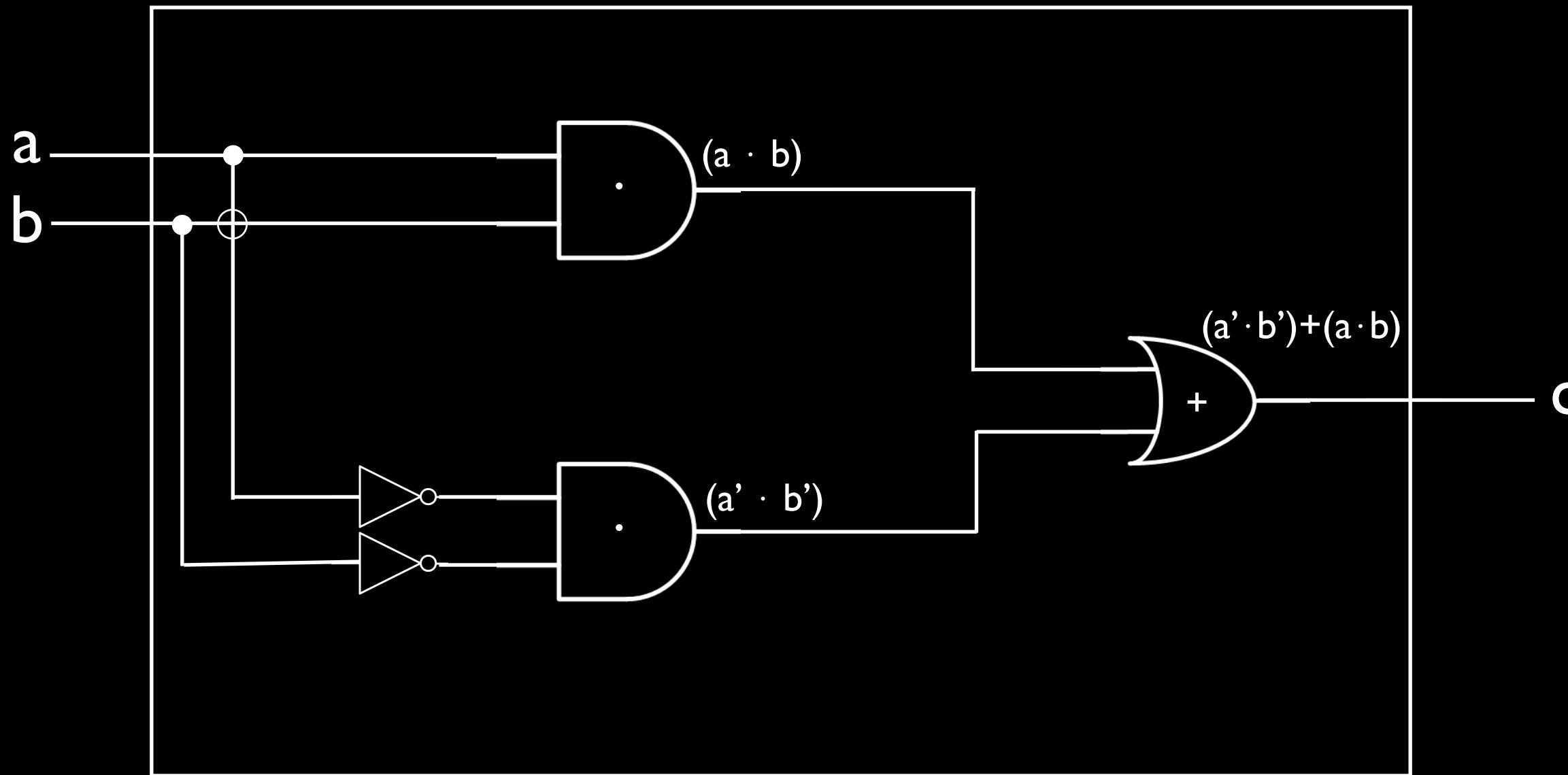


4-Bit Compare for Equality (CE)

input

 


output


4-Bit Compare for Equality (CE)

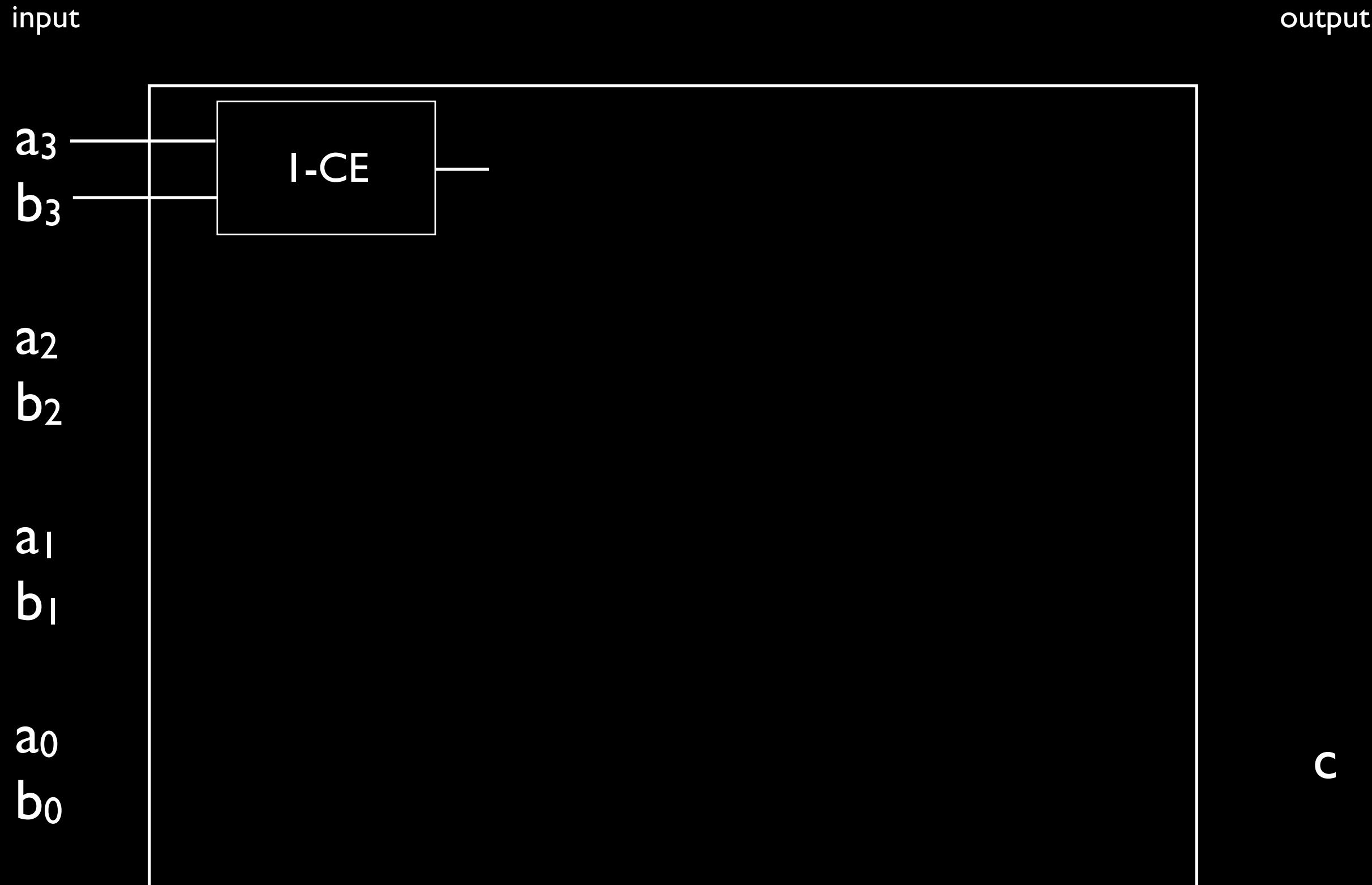


4-Bit Compare for Equality (CE)

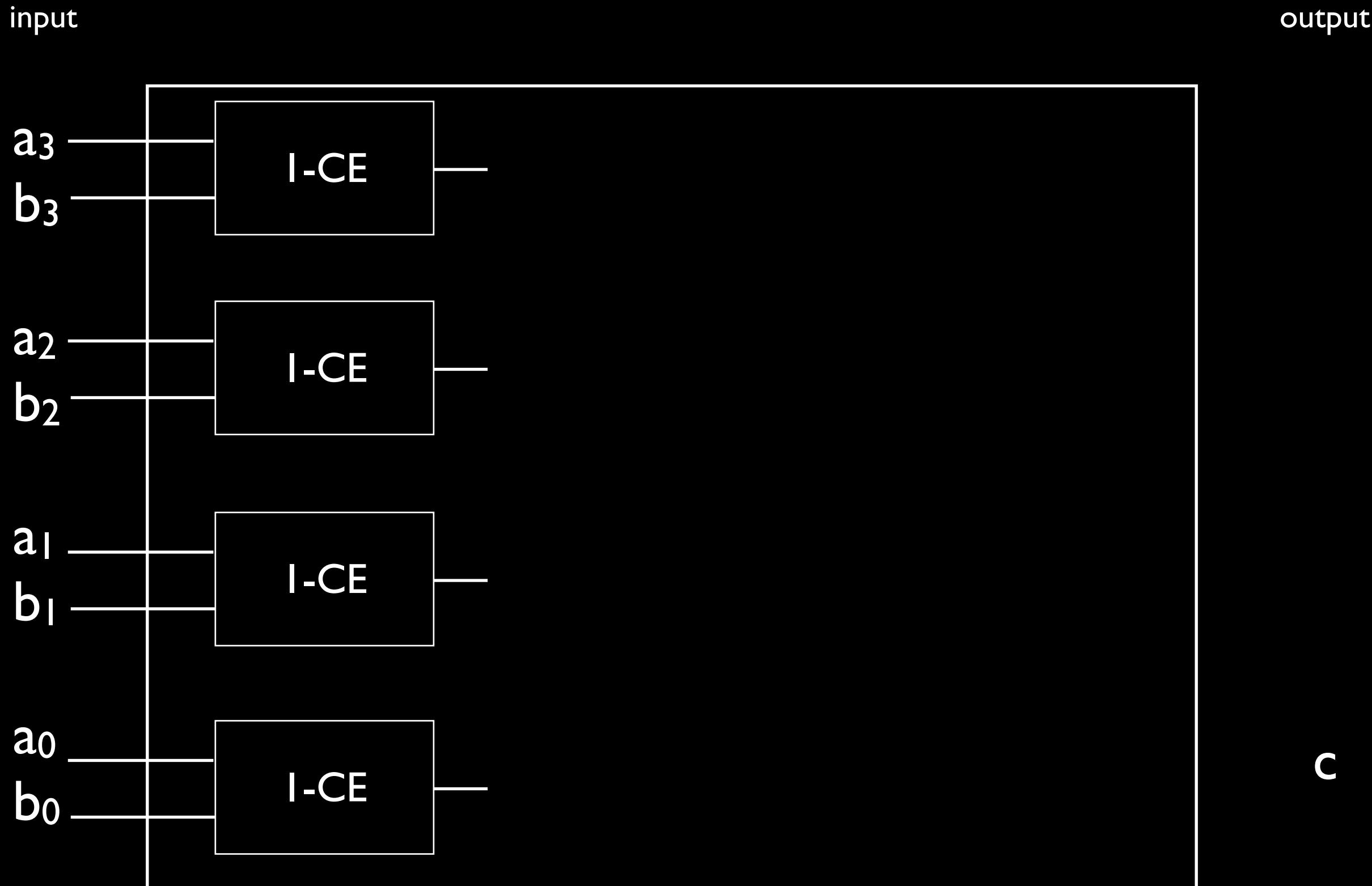


4-Bit Compare for Equality (CE)

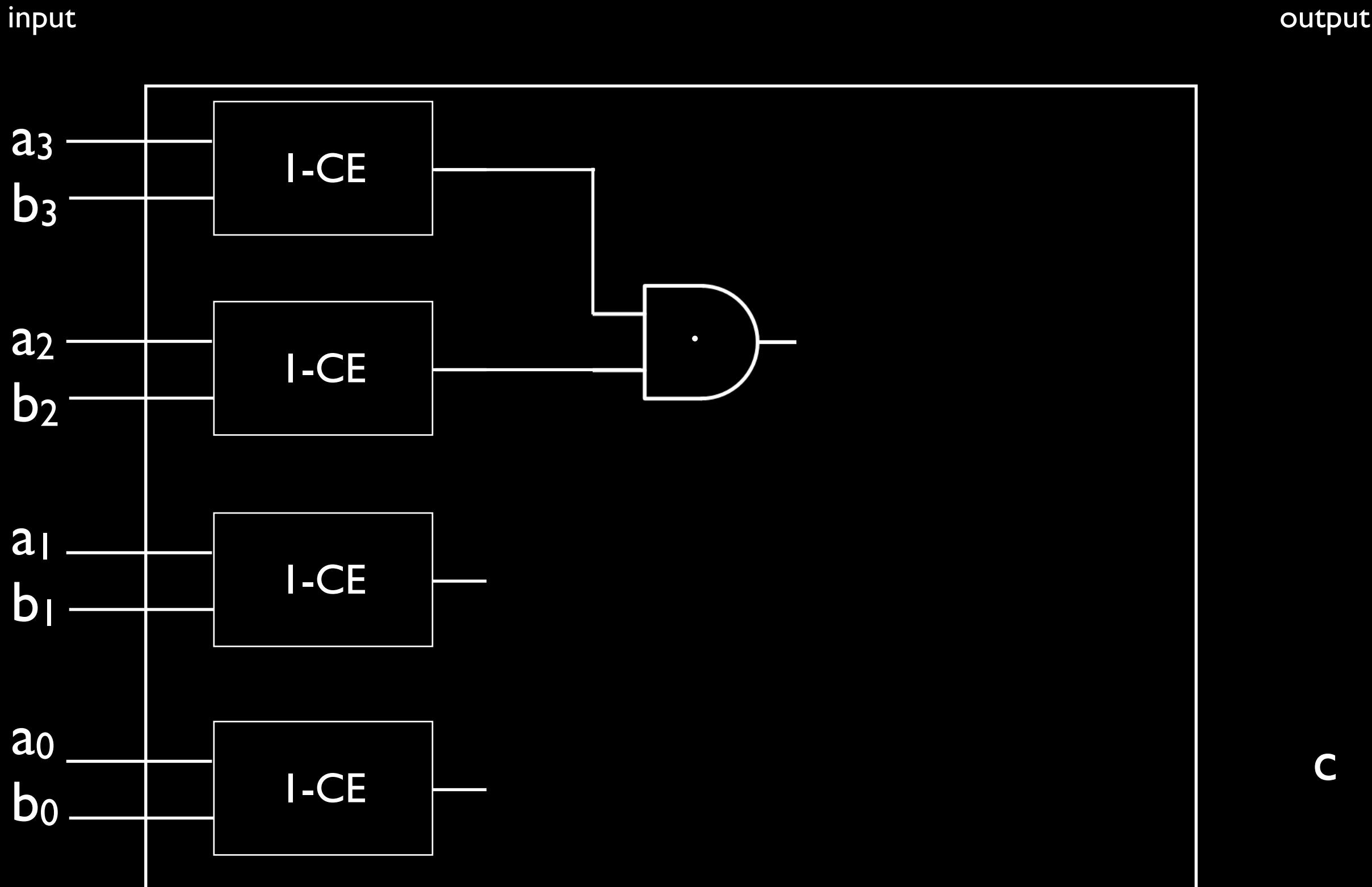

4-Bit Compare for Equality (CE)

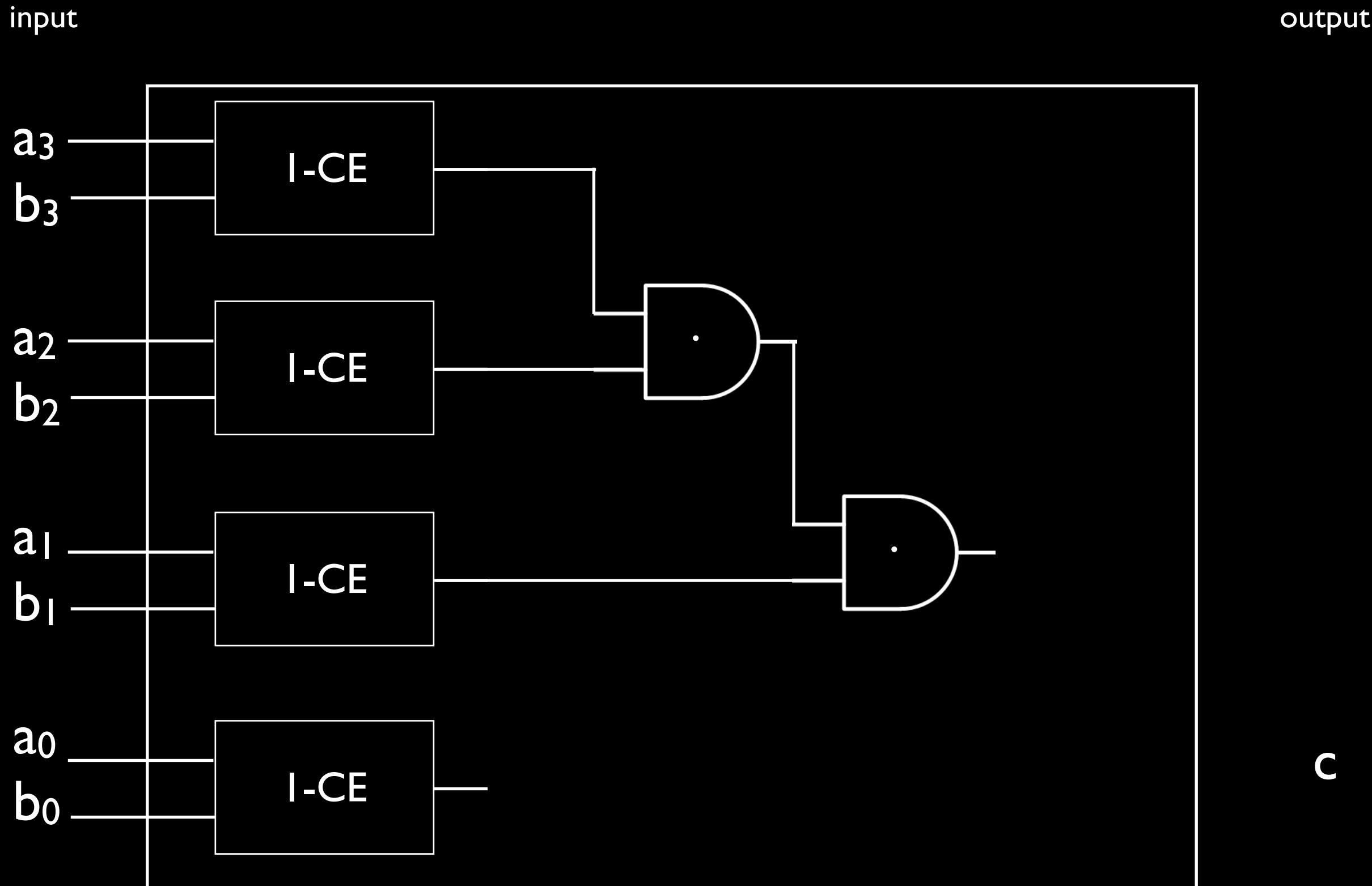

4-Bit Compare for Equality (CE)

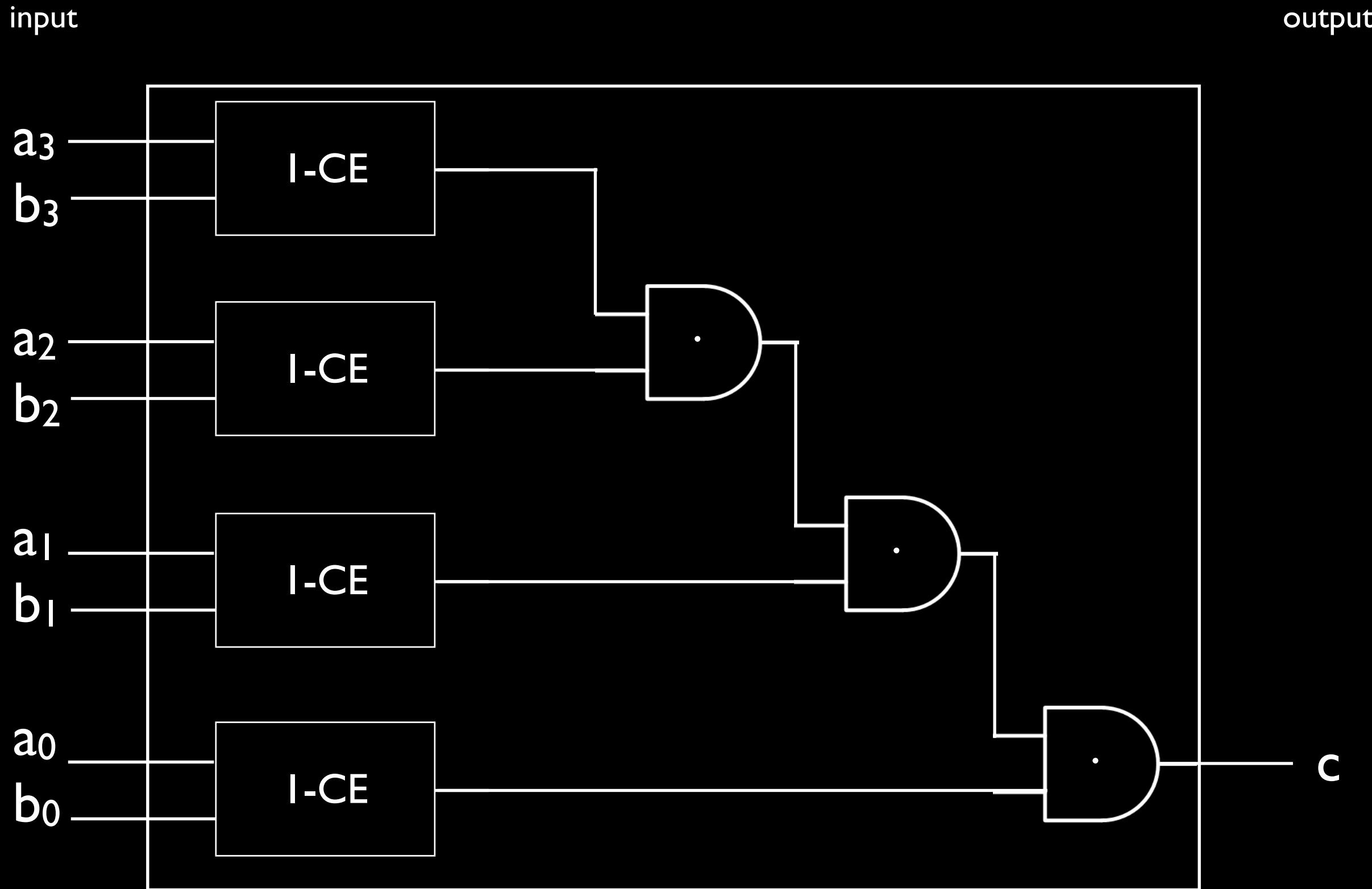

I-Bit Adder

build a circuit that adds two I-bit numbers

I-Bit Adder

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = ?$$

I-Bit Adder

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10 \quad \textit{need to carry}$$

I-Bit Adder

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$

input: two digits a, b

I-Bit Adder

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$

input: two digits a, b and a carry c

I-Bit Adder

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$

output: sum d and carry e

I-Bit Adder

$$\begin{array}{r} 5 \\ 1 \\ \hline \end{array} \quad \begin{array}{r} 101 \\ 001 \\ \hline \end{array} \quad \begin{array}{l} 2^2 + 2^0 \\ 2^0 \end{array}$$

6

I-Bit Adder

$$\begin{array}{r} & & 1 \\ 5 & & 101 \\ 1 & & 001 \\ \hline - & & - \\ 6 & & 0 \end{array}$$

I-Bit Adder

$$\begin{array}{r} & & 1 \\ 5 & & 101 \\ 1 & & 001 \\ \hline - & & - \\ 6 & & 10 \end{array}$$

I-Bit Adder

$$\begin{array}{r} & & 1 \\ 5 & & 101 \\ 1 & & 001 \\ \hline - & & - \\ 6 & & 110 \end{array}$$

1-Bit Adder

$$\begin{array}{r} & & 1 \\ 5 & & 101 \\ 1 & & 001 \\ \hline - & & - \\ 6 & & 110 \end{array} \quad 2^2 + 2^1$$

I-Bit Adder

input: digits a, b and carry c

output: sum d and carry e

I-Bit Adder

a	b	c	d	e
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

input: digits a, b and carry c
output: sum d and carry e

I-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

input: digits a, b and carry c
output: sum d and carry e

I-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

input: digits a, b and carry c
output: sum d and carry e

I-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

input: digits a, b and carry c
output: sum d and carry e

I-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0		
1	0	1		
1	1	0		
1	1	1		

input: digits a, b and carry c
output: sum d and carry e

I-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1		
1	1	0		
1	1	1		

input: digits a, b and carry c
output: sum d and carry e

I-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0		
1	1	1		

input: digits a, b and carry c
output: sum d and carry e

I-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1		

input: digits a, b and carry c
output: sum d and carry e

I-Bit Adder

a	b	c	d	e
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

input: digits a, b and carry c
output: sum d and carry e

I-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0		
0	1	0	1	0		
0	1	1	0	1		
1	0	0	1	0		
1	0	1	0	1		
1	1	0	0	1		
1	1	1	1	1		

I-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0		
0	1	0	1	0		
0	1	1	0	1		
1	0	0	1	0		
1	0	1	0	1		
1	1	0	0	1		
1	1	1	1	1		

I-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0		
0	1	1	0	1		
1	0	0	1	0		
1	0	1	0	1		
1	1	0	0	1		
1	1	1	1	1		

I-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0	$a' \cdot b \cdot c'$	
0	1	1	0	1		
1	0	0	1	0		
1	0	1	0	1		
1	1	0	0	1		
1	1	1	1	1		

I-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0	$a' \cdot b \cdot c'$	
0	1	1	0	1		
1	0	0	1	0	$a \cdot b' \cdot c'$	
1	0	1	0	1		
1	1	0	0	1		
1	1	1	1	1		

I-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0	$a' \cdot b \cdot c'$	
0	1	1	0	1		
1	0	0	1	0	$a \cdot b' \cdot c'$	
1	0	1	0	1		
1	1	0	0	1		
1	1	1	1	1	$a \cdot b \cdot c$	

I-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0	$a' \cdot b \cdot c'$	
0	1	1	0	1		$a' \cdot b \cdot c$
1	0	0	1	0	$a \cdot b' \cdot c'$	
1	0	1	0	1		$a \cdot b' \cdot c$
1	1	0	0	1		$a \cdot b \cdot c'$
1	1	1	1	1	$a \cdot b \cdot c$	$a \cdot b \cdot c$

I-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0	$a' \cdot b \cdot c'$	
0	1	1	0	1		$a' \cdot b \cdot c$
1	0	0	1	0	$a \cdot b' \cdot c'$	
1	0	1	0	1		$a \cdot b' \cdot c$
1	1	0	0	1		$a \cdot b \cdot c'$
1	1	1	1	1	$a \cdot b \cdot c$	$a \cdot b \cdot c$


$$d = (a' \cdot b' \cdot c) + (a' \cdot b \cdot c') + (a \cdot b' \cdot c') + (a \cdot b \cdot c)$$

I-Bit Adder

a	b	c	d	e	sub-expressions (d)	sub-expressions (e)
0	0	0	0	0		
0	0	1	1	0	$a' \cdot b' \cdot c$	
0	1	0	1	0	$a' \cdot b \cdot c'$	
0	1	1	0	1		$a' \cdot b \cdot c$
1	0	0	1	0	$a \cdot b' \cdot c'$	
1	0	1	0	1		$a \cdot b' \cdot c$
1	1	0	0	1		$a \cdot b \cdot c'$
1	1	1	1	1	$a \cdot b \cdot c$	$a \cdot b \cdot c$

$$e = (a' \cdot b \cdot c) + (a \cdot b' \cdot c) + (a \cdot b \cdot c') + (a \cdot b \cdot c)$$


1-Bit Adder

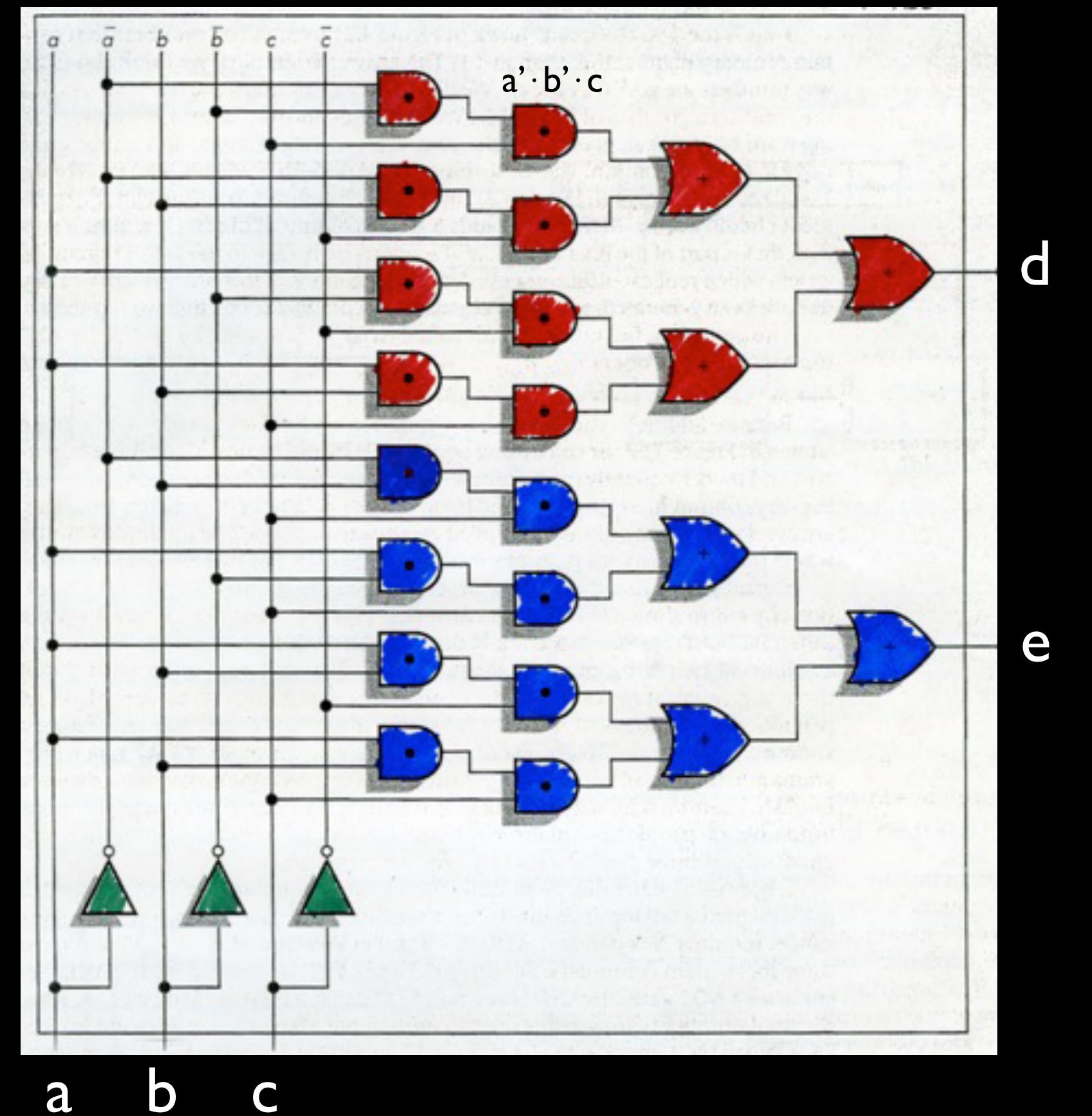


4-Bit Adder

build a circuit that adds two 4-bit numbers


4-Bit Adder

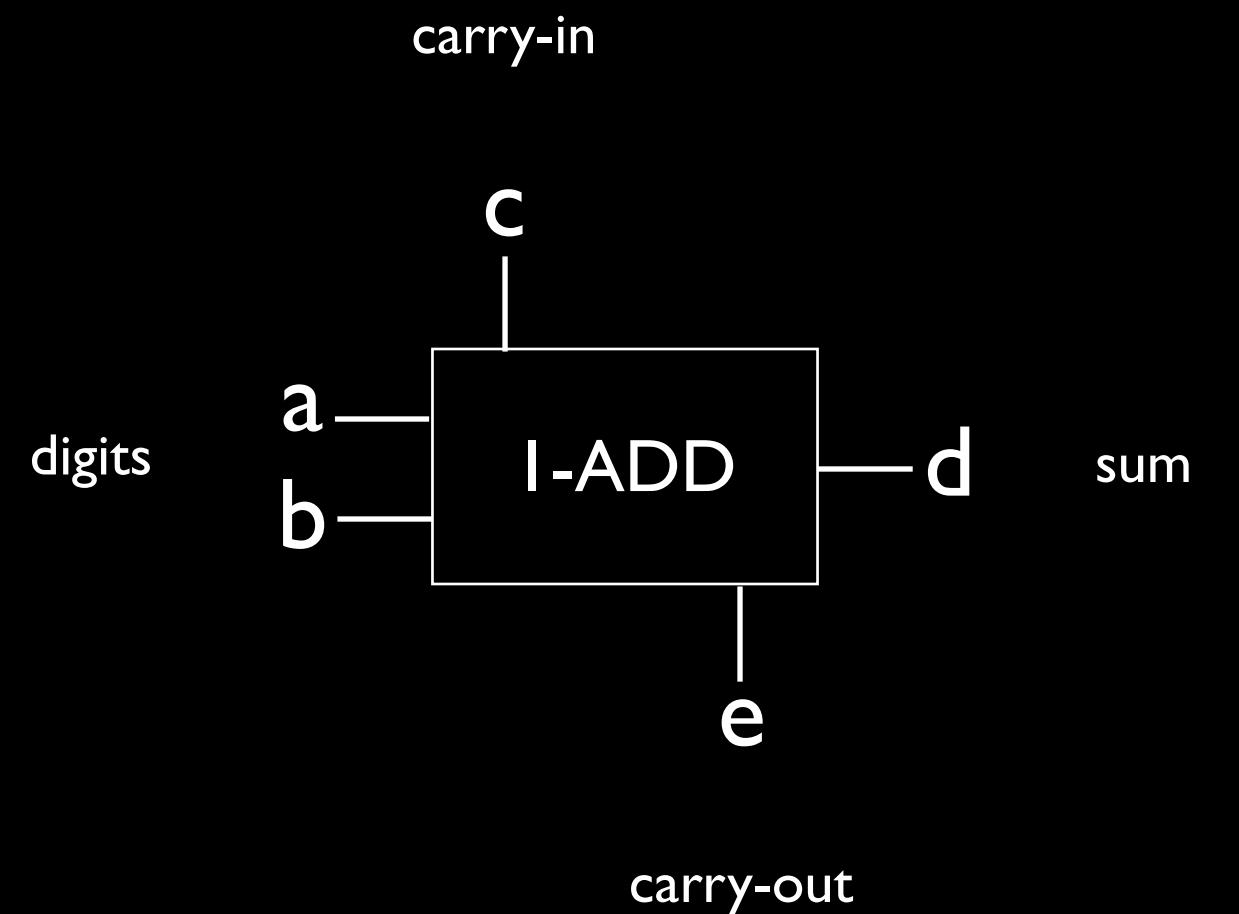


4-Bit Adder

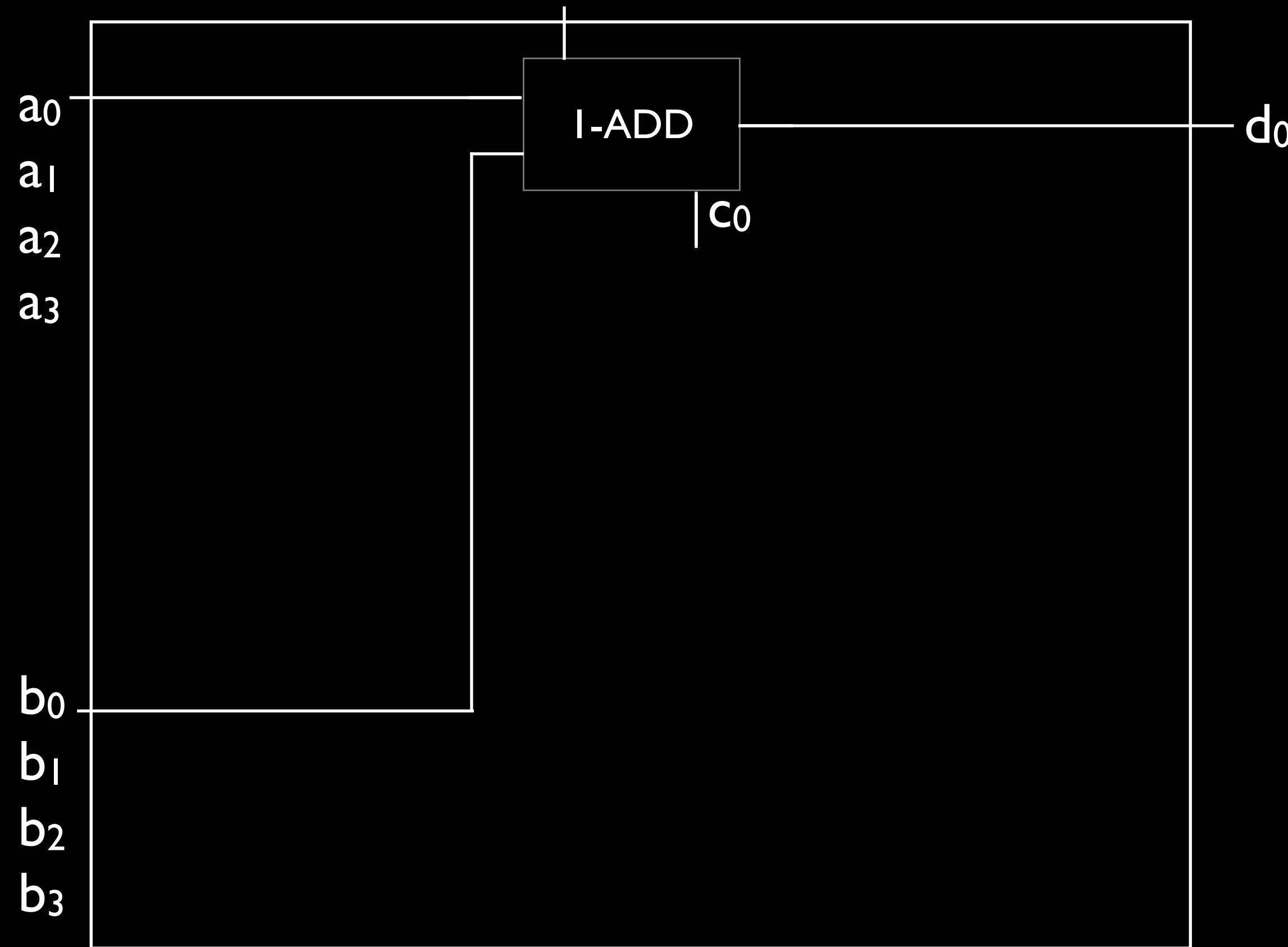


4-Bit Adder

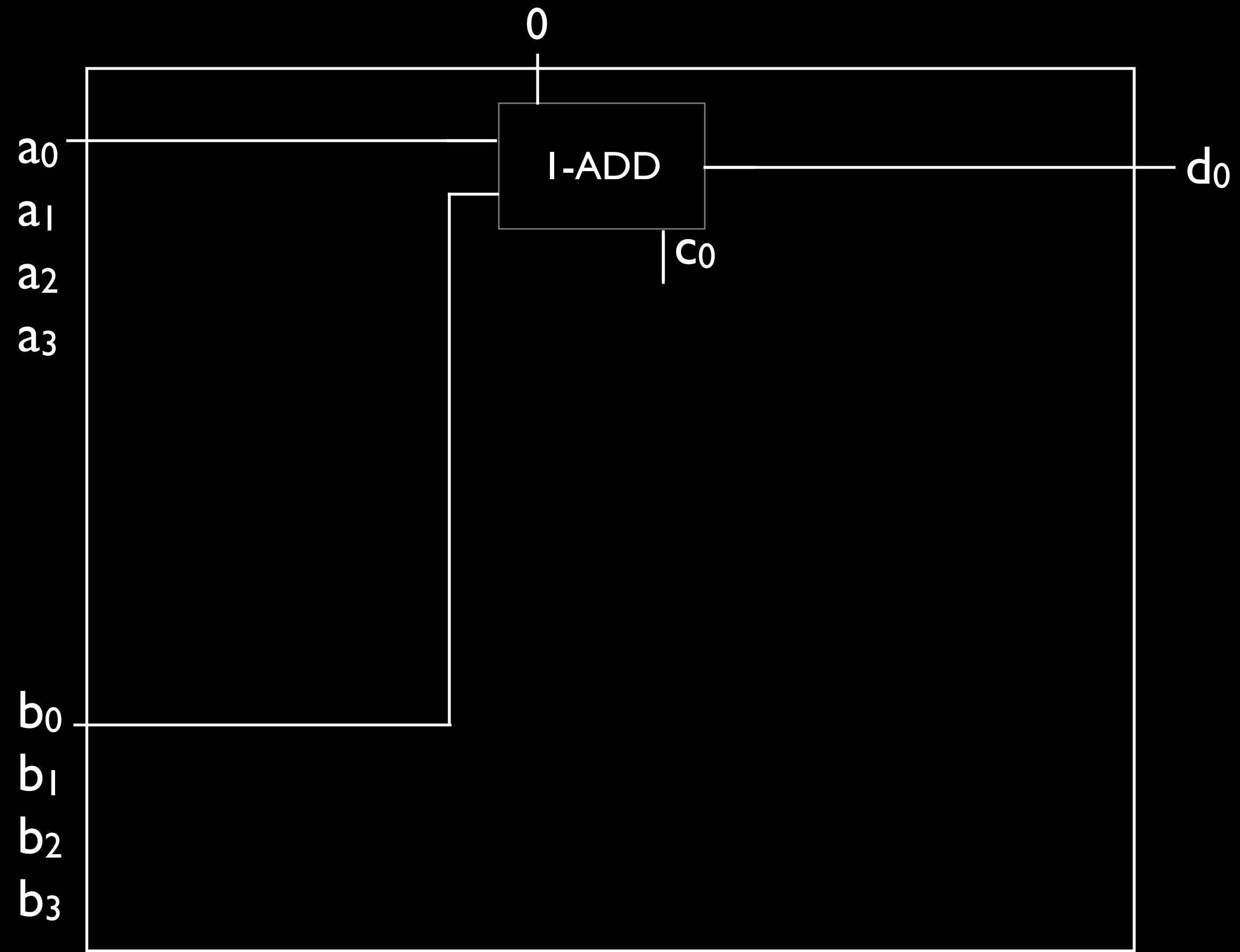


4-Bit Adder

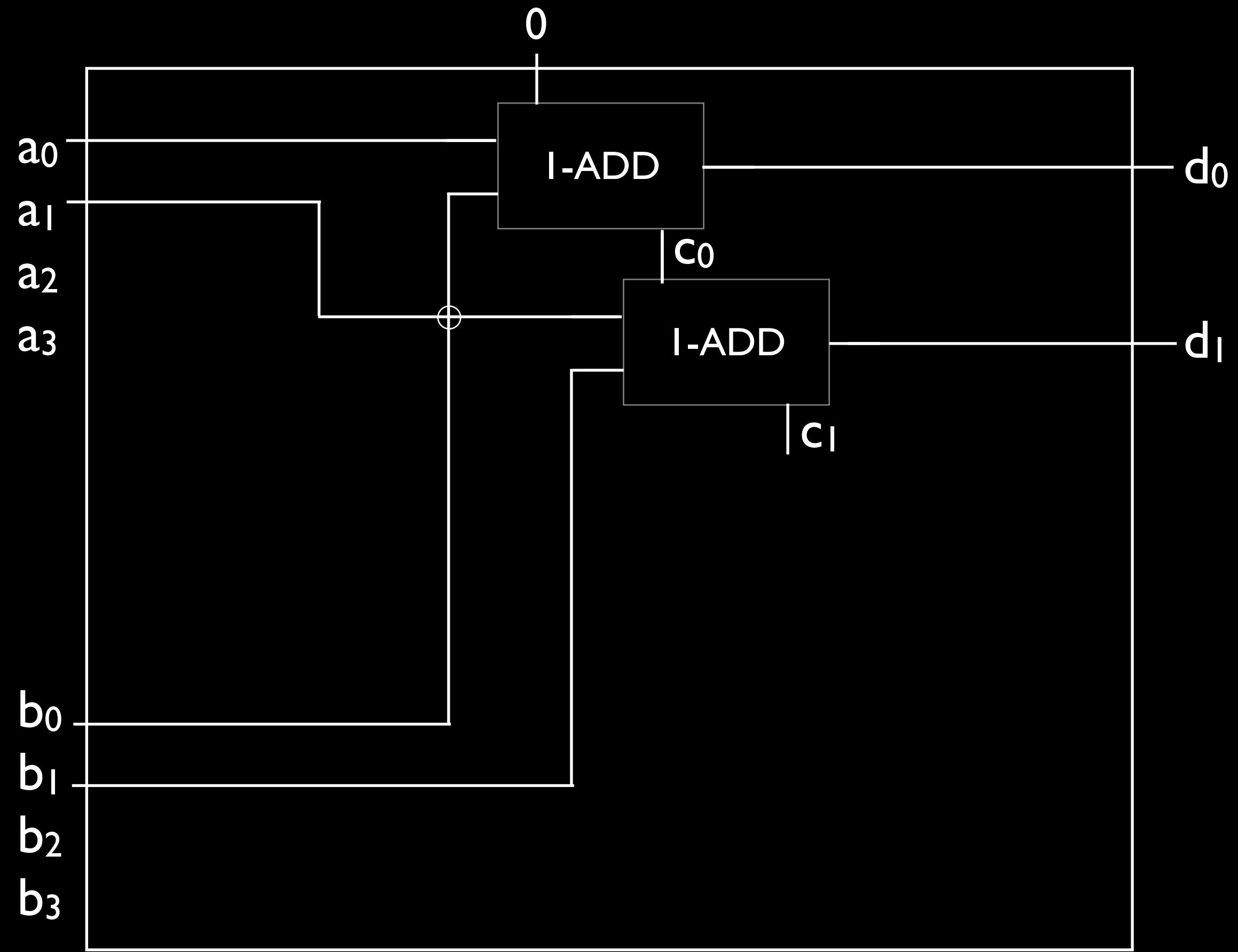

4-Bit Adder

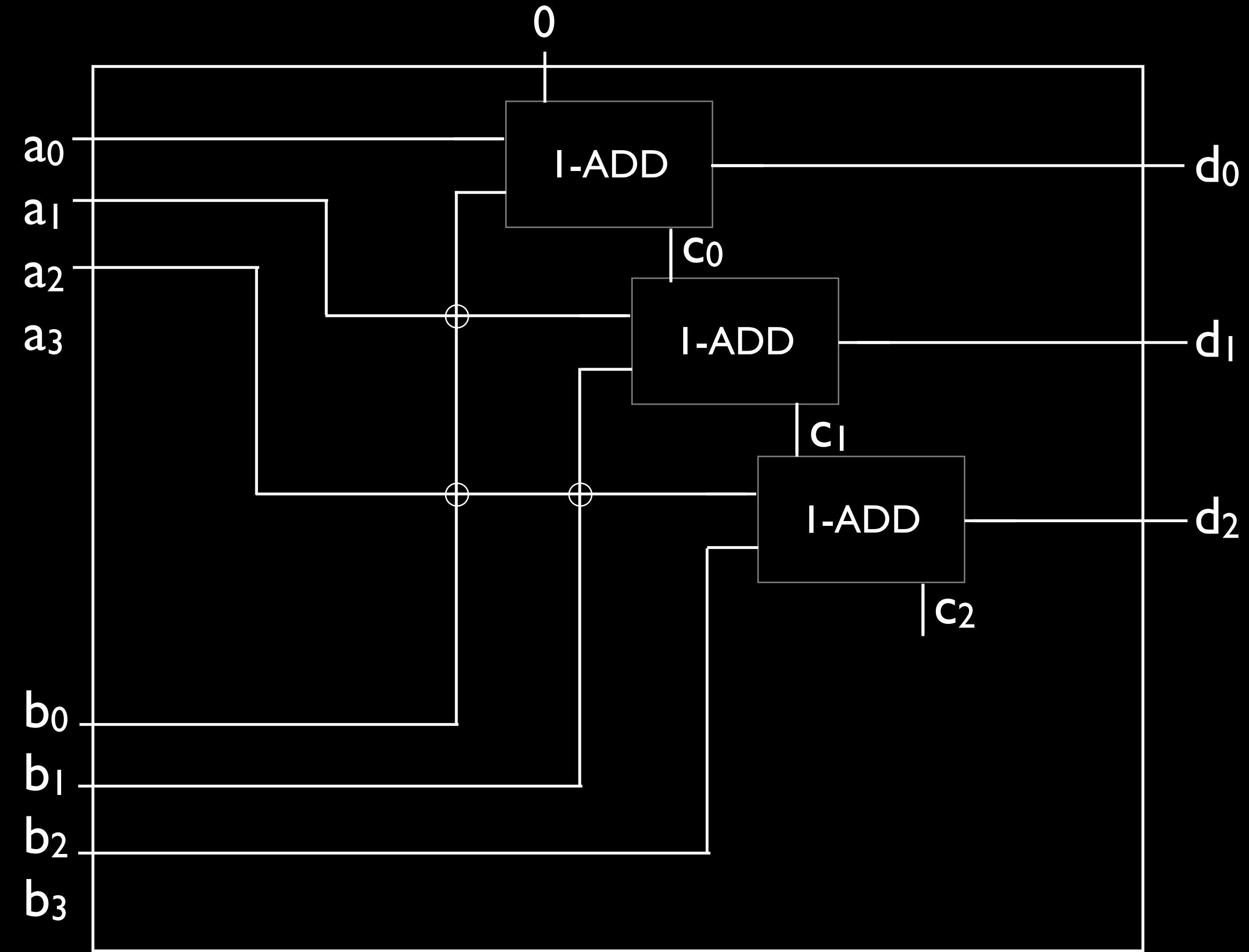

4-Bit Adder

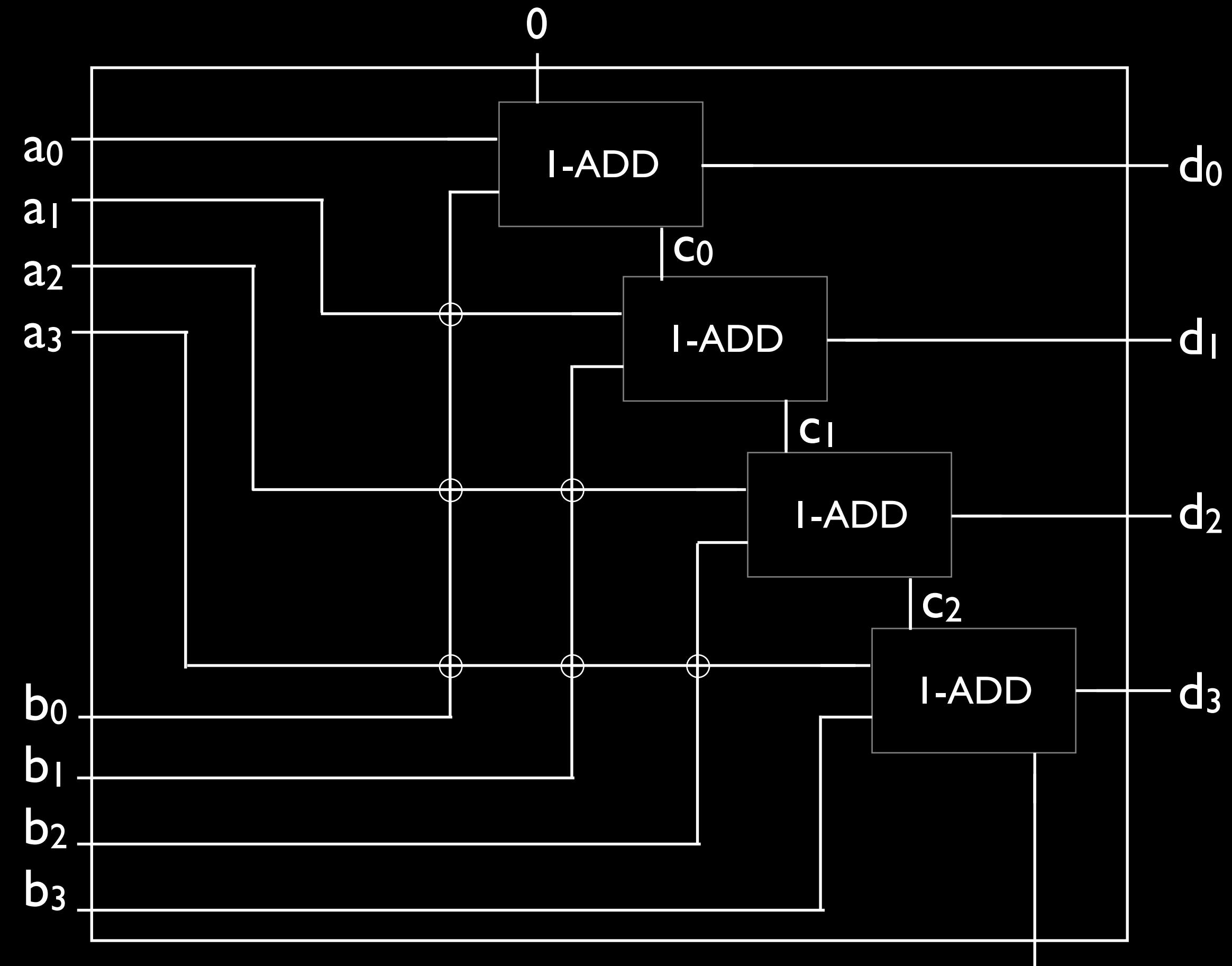


32-bit Adder

$96 = 32 \times 3$ not gates

$512 = 32 \times 16$ and gates

$192 = 32 \times 6$ or gates

800 gates

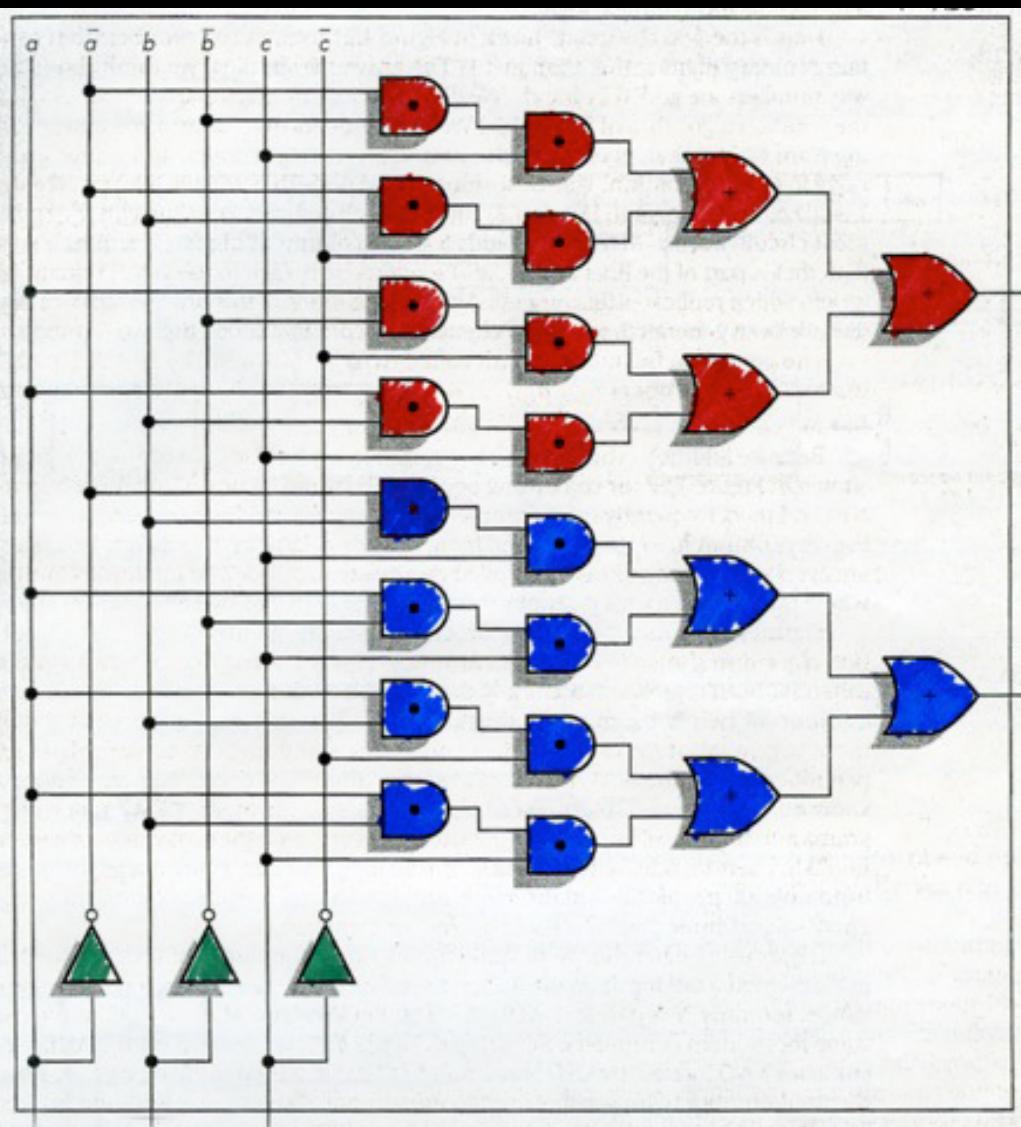

32-bit Adder


$96 = 32 \times 3$ not gates

$512 = 32 \times 16$ and gates

$192 = 32 \times 6$ or gates

800 gates

$1,504 = 96 + 1024 + 384$ transistors

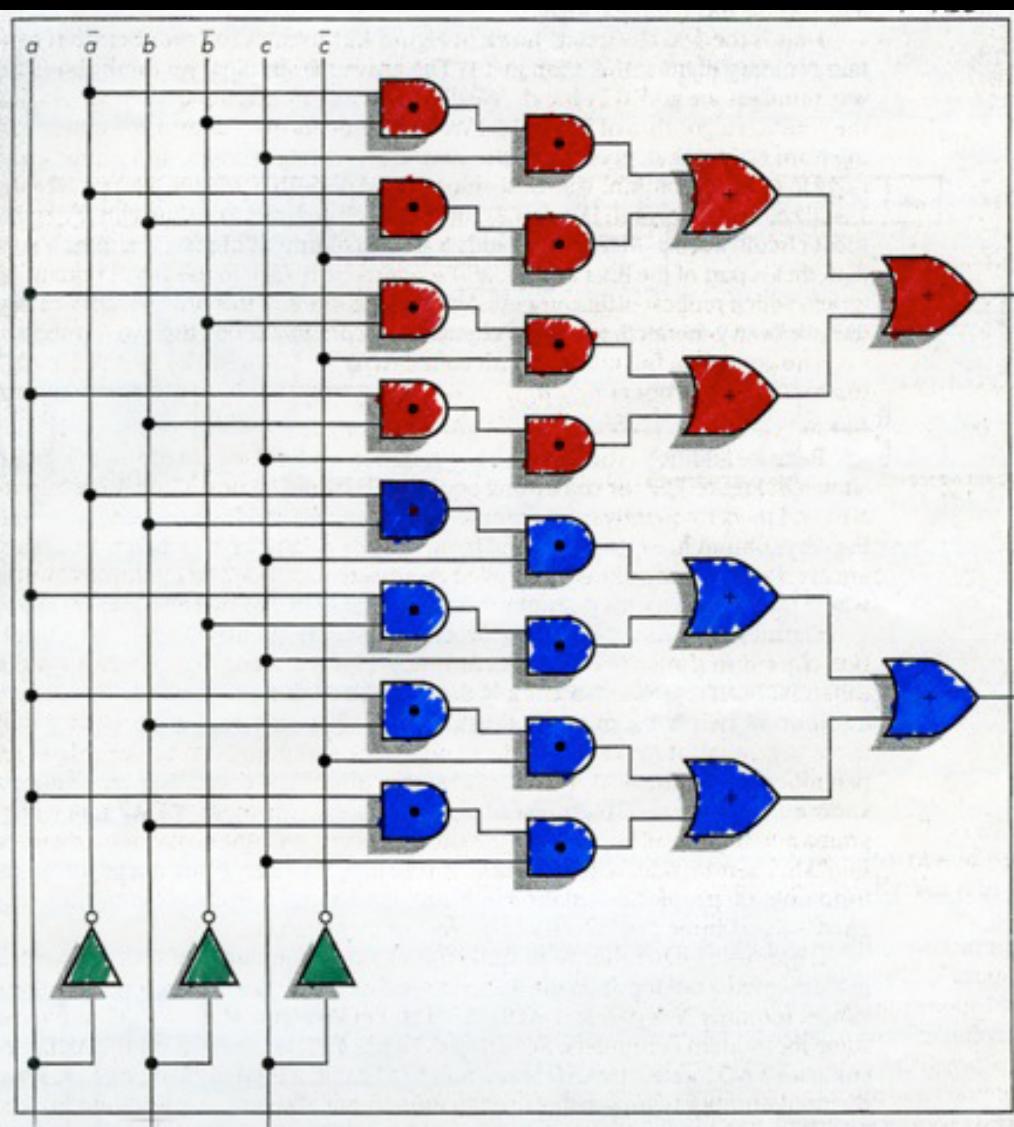

32-bit Adder

$96 = 32 \times 3$ not gates

$512 = 32 \times 16$ and gates


$192 = 32 \times 6$ or gates

800 gates

$1,504 = 96 + 1024 + 384$ transistors

1945: refrigerator-sized computer

2015: .-sized computer

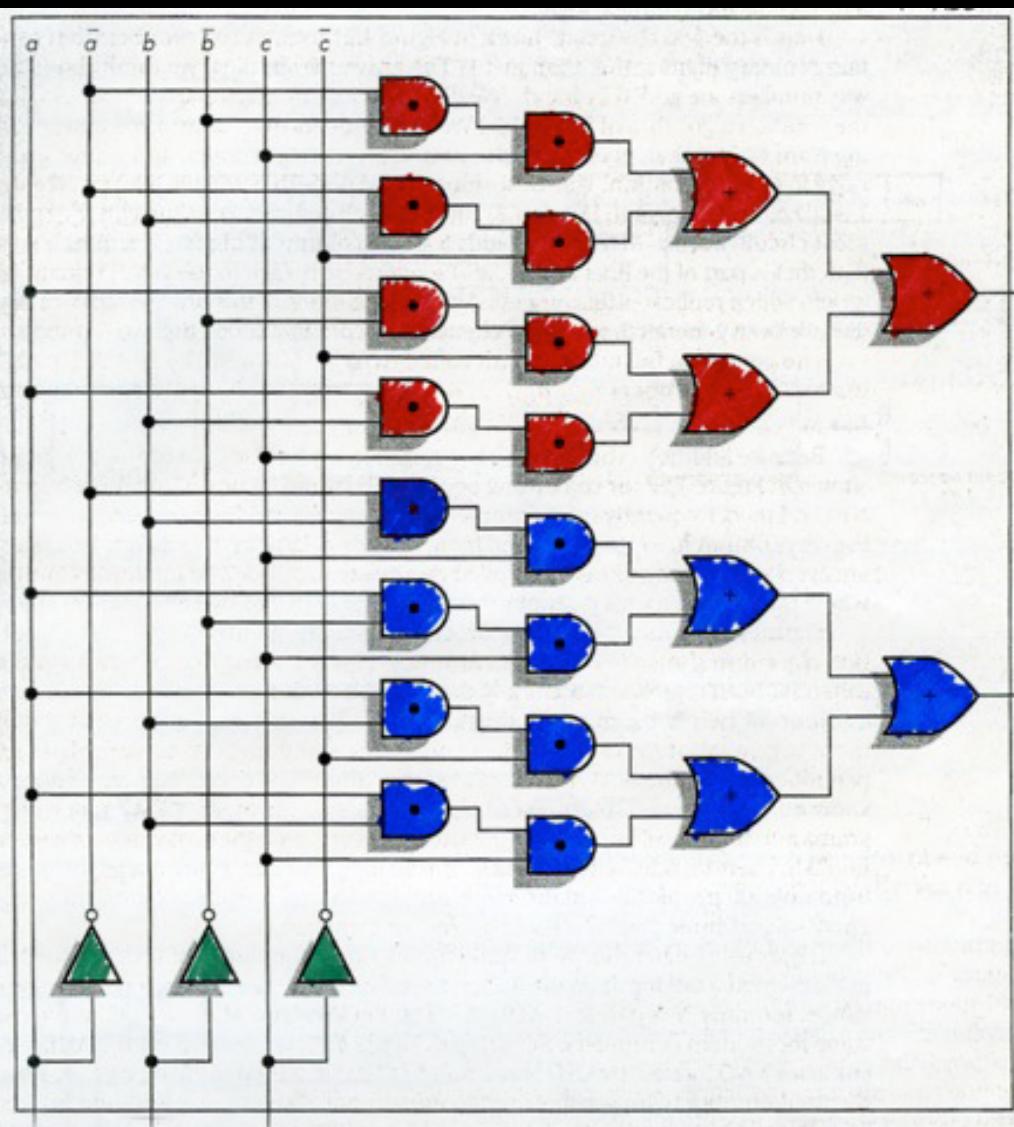

Equals 0

build a circuit that determines if an 8-bit number is 0

Equals 0

$$a_7 \ a_6 \ a_5 \ a_4 \ a_3 \ a_2 \ a_1 \ a_0 = 00000000$$

Equals 0

									output
a	b	c	d	e	f	g	h	i	
⋮									⋮
⋮									⋮
⋮									⋮

How many rows?

Equals 0

a	b	c	d	e	f	g	h	i
0	0	0	0	0	0	0	0	I


Only one row has an output of I

Equals 0


a	b	c	d	e	f	g	h	i
0	0	0	0	0	0	0	0	l

$$i = a' \cdot b' \cdot c' \cdot d' \cdot e' \cdot f' \cdot g' \cdot h'$$


Equals 0

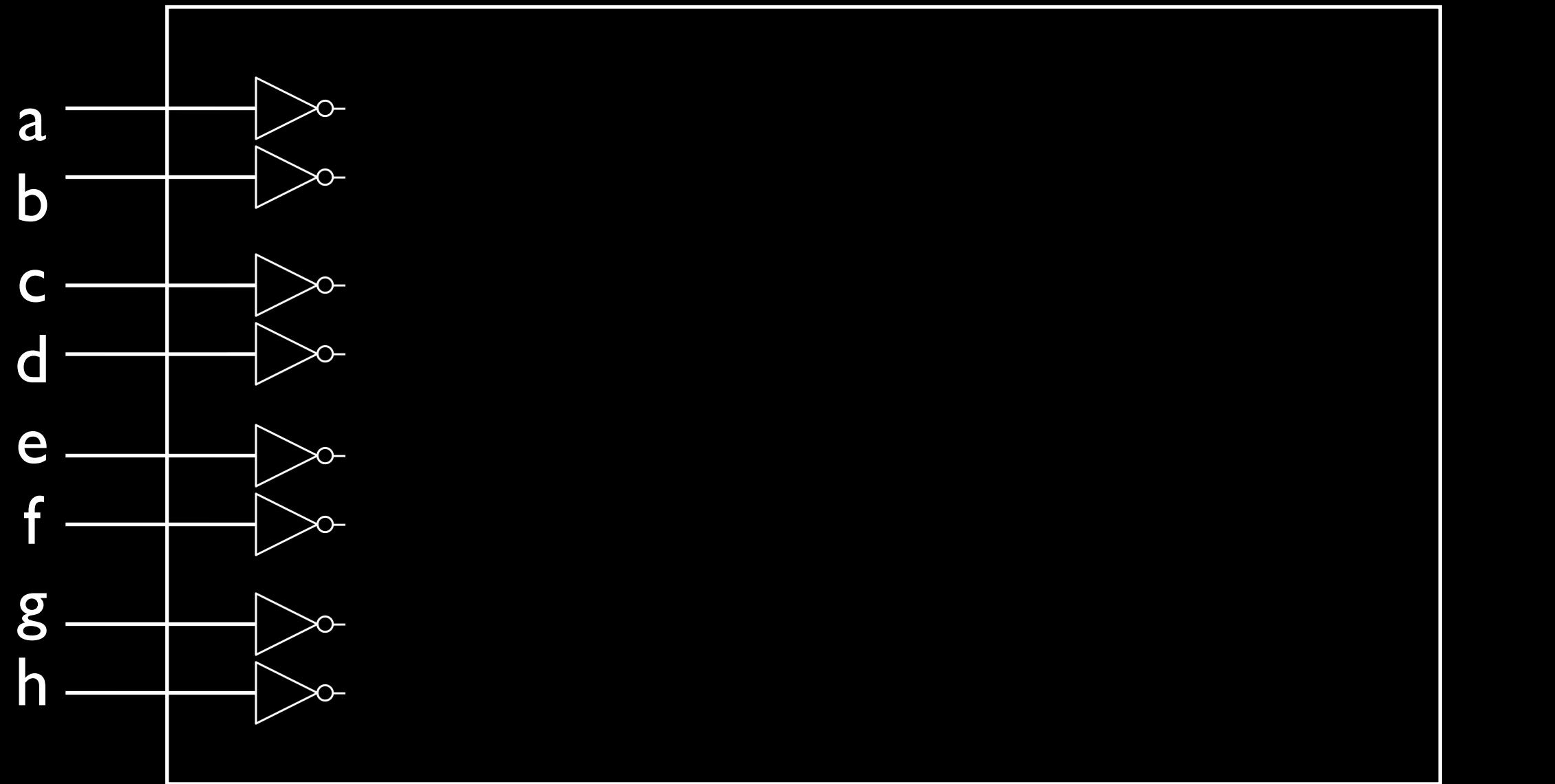

Equals 0

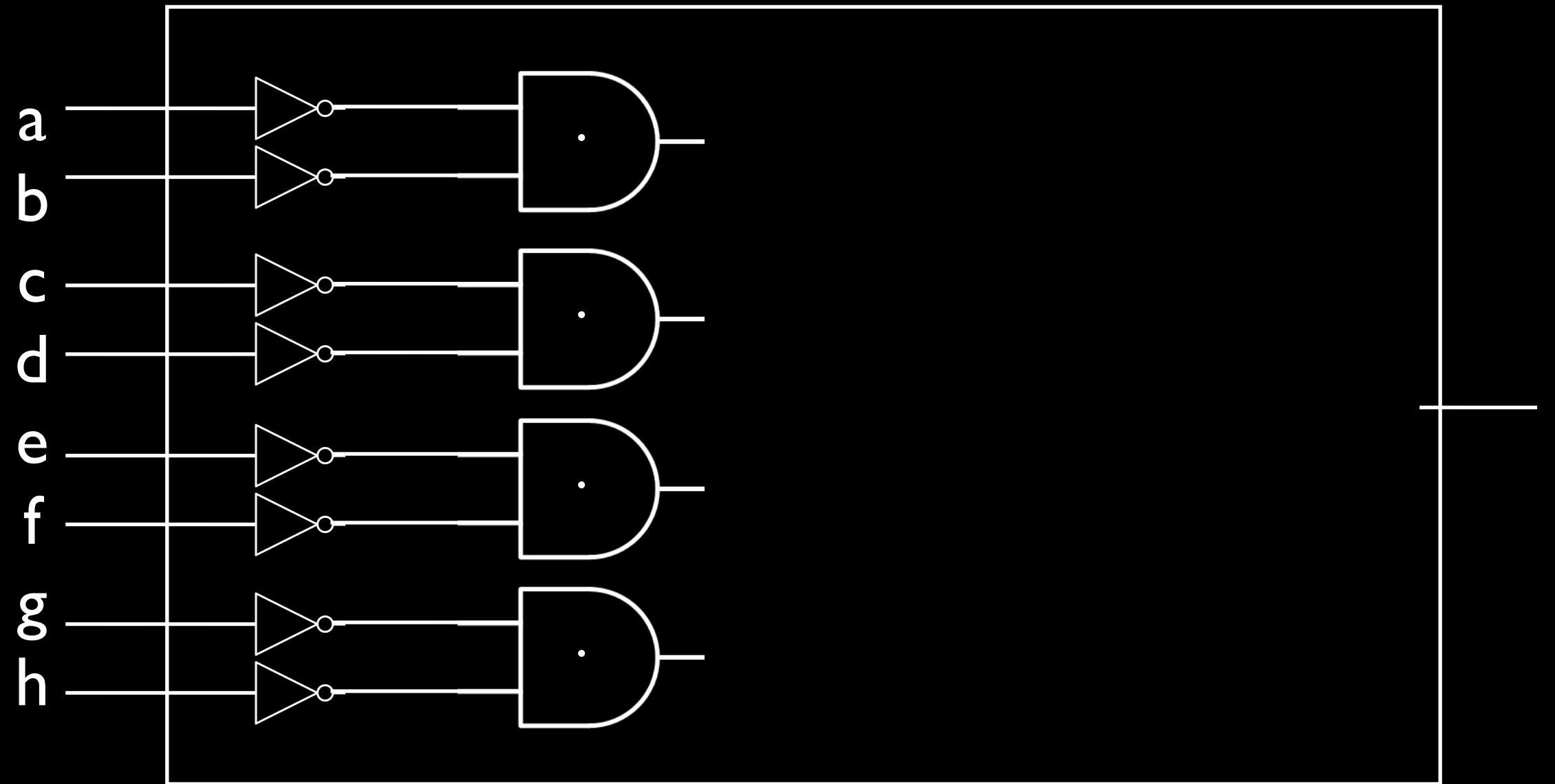

Equals 0

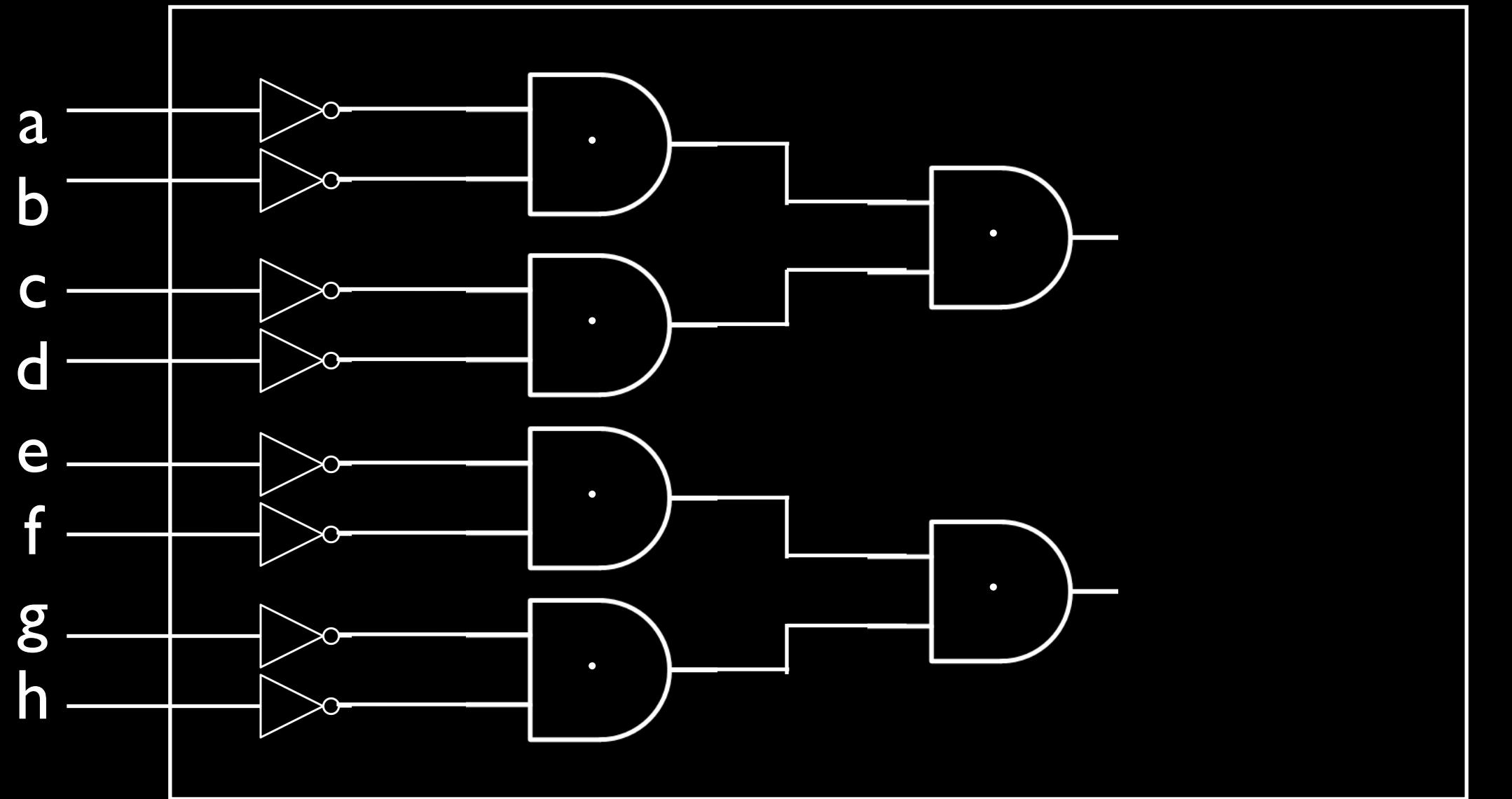

i

Equals 0

